
#### Chapter 11, Solution 1.

$$\begin{aligned} v(t) &= 160\cos(50t) \\ i(t) &= -20\sin(50t - 30^\circ) = 2\cos(50t - 30^\circ + 180^\circ - 90^\circ) \\ i(t) &= 20\cos(50t + 60^\circ) \\ p(t) &= v(t)i(t) = (160)(20)\cos(50t)\cos(50t + 60^\circ) \\ p(t) &= 1600 \big[\cos(100t + 60^\circ) + \cos(60^\circ)\big] \, W \\ p(t) &= \mathbf{800} + \mathbf{1600}\cos(\mathbf{100t} + \mathbf{60}^\circ) \, W \\ P &= \frac{1}{2} \, V_m \, I_m \, \cos(\theta_v - \theta_i) = \frac{1}{2} (160)(20)\cos(60^\circ) \\ P &= \mathbf{800} \, \, W \end{aligned}$$
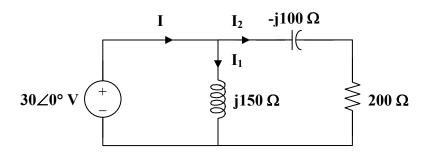
#### Chapter 11, Solution 2.

First, transform the circuit to the frequency domain.



$$I_1 = \frac{30 \angle 0^{\circ}}{\text{j}150} = 0.2 \angle -90^{\circ} = -\text{j}0.2$$

$$i_1(t) = 0.2\cos(500t - 90^\circ) = 0.2\sin(500t)$$

$$\mathbf{I}_2 = \frac{30 \angle 0^{\circ}}{200 - j100} = \frac{0.3}{2 - j} = 0.1342 \angle 26.56^{\circ} = 0.12 + j0.06$$

$$i_2(t) = 0.1342\cos(500t + 25.56^\circ)$$
  
 $\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2 = 0.12 - j0.14 = 0.1844 \angle -49.4^\circ$   
 $i(t) = 0.1844\cos(500t - 35^\circ)$ 

For the voltage source,

$$p(t) = v(t)i(t) = [30\cos(500t)] \times [0.1844\cos(500t - 35^{\circ})]$$

At 
$$t = 2 s$$
,  $p = 5.532 \cos(1000) \cos(1000 - 35^{\circ})$   
 $p = (5.532)(0.5624)(0.935)$   
 $p = 2.91 \text{ W}$ 

For the inductor,

$$p(t) = v(t)i(t) = [30\cos(500t)] \times [0.2\sin(500t)]$$

At 
$$t = 2 s$$
,  $p = 6 cos(1000) sin(1000)$   
 $p = (6)(0.5624)(0.8269)$   
 $p = 2.79 W$ 

For the capacitor,

$$\mathbf{V}_{c} = \mathbf{I}_{2} (-j100) = 13.42 \angle -63.44^{\circ}$$

$$p(t) = v(t)i(t) = [13.42\cos(500 - 63.44^{\circ})] \times [0.1342\cos(500t + 25.56^{\circ})]$$

At 
$$t = 2 \text{ s}$$
,  $p = 18 \cos(1000 - 63.44^{\circ}) \cos(1000 + 26.56^{\circ})$   
 $p = (18)(0.991)(0.1329)$   
 $p = 2.37 \text{ W}$ 

For the resistor,

$$\begin{aligned} \mathbf{V}_{R} &= 200\,\mathbf{I}_{2} = 26.84 \angle 25.56^{\circ} \\ p(t) &= v(t)\,i(t) = [26.84\cos(500t + 26.56^{\circ})] \times [0.1342\cos(500t + 26.56^{\circ})] \end{aligned}$$


At 
$$t = 2 s$$
,  $p = 3.602 \cos^2(1000 + 25.56^\circ)$   
 $p = (3.602)(0.1329^2)$   
 $p = \mathbf{0.0636 W}$ 

#### Chapter 11, Solution 3.

$$10\cos(2t+30^{\circ}) \longrightarrow 10\angle 30^{\circ}, \qquad \omega = 2$$

$$1 \text{ H } \longrightarrow j\omega L = j2$$
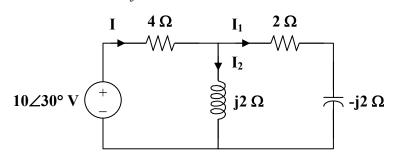
$$0.25 \text{ F} \longrightarrow \frac{1}{\text{j}\omega\text{C}} = -\text{j}2$$



$$j2 \parallel (2 - j2) = \frac{(j2)(2 - j2)}{2} = 2 + j2$$

$$\mathbf{I} = \frac{10 \angle 30^{\circ}}{4 + 2 + \mathrm{i}2} = 1.581 \angle 11.565^{\circ}$$

$$I_1 = \frac{j2}{2}I = jI = 1.581 \angle 101.565^{\circ}$$

$$\mathbf{I}_2 = \frac{2 - j2}{2}\mathbf{I} = 2.236 \angle 56.565^{\circ}$$

For the source,

$$\mathbf{S} = \mathbf{V} \mathbf{I}^* = \frac{1}{2} (10 \angle 30^\circ) (1.581 \angle -11.565^\circ)$$

$$S = 7.905 \angle 18.43^{\circ} = 7.5 + j2.5$$

The average power supplied by the source = 7.5 W

For the 4- $\Omega$  resistor, the average power absorbed is

$$P = \frac{1}{2} |\mathbf{I}|^2 R = \frac{1}{2} (1.581)^2 (4) = \mathbf{5} \mathbf{W}$$

For the inductor,

$$\mathbf{S} = \frac{1}{2} |\mathbf{I}_2|^2 \mathbf{Z}_L = \frac{1}{2} (2.236)^2 (j2) = j5$$

The average power absorbed by the inductor = 0 W

For the 2- $\Omega$  resistor, the average power absorbed is


$$P = \frac{1}{2} |I_1|^2 R = \frac{1}{2} (1.581)^2 (2) = \underline{2.5 \text{ W}}$$

For the capacitor,

$$\mathbf{S} = \frac{1}{2} |\mathbf{I}_1|^2 \mathbf{Z}_c = \frac{1}{2} (1.581)^2 (-j2) = -j2.5$$

The average power absorbed by the capacitor  $= \mathbf{0} \mathbf{W}$ 

# Chapter 11, Solution 4.

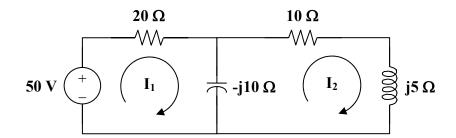

For mesh 1,

$$50 = (20 - j10) \mathbf{I}_1 + j10 \mathbf{I}_2$$
  

$$5 = (2 - j) \mathbf{I}_1 + j \mathbf{I}_2$$
(1)

For mesh 2,

$$0 = (10 + j5 - j10) \mathbf{I}_{2} + j10 \mathbf{I}_{1}$$
  

$$0 = (2 - j) \mathbf{I}_{2} + j2 \mathbf{I}_{1}$$
(2)

In matrix form,

$$\begin{bmatrix} 5 \\ 0 \end{bmatrix} = \begin{bmatrix} 2 - \mathbf{j} & \mathbf{j} \\ \mathbf{j} 2 & 2 - \mathbf{j} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$

$$\Delta = 5 - j4$$
,  $\Delta_1 = 5(2 - j)$ ,  $\Delta_2 = -j10$ 

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{5(2-j)}{5-j4} = 1.746 \angle 12.1^\circ$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-j10}{5 - j4} = 1.562 \angle 128.66^\circ$$

For the source,

$$\mathbf{S} = \frac{1}{2} \mathbf{V} \mathbf{I}_{1}^{*} = 43.65 \angle -12.1^{\circ}$$

The average power supplied =  $43.65 \cos(12.1^{\circ}) = 42.68 \text{ W}$ 

For the  $20-\Omega$  resistor,

$$P = \frac{1}{2} |I_1|^2 R = \underline{30.48 W}$$

For the inductor and capacitor,


$$P = 0 W$$

For the  $10-\Omega$  resistor,

$$P = \frac{1}{2} |I_2|^2 R = \underline{12.2 W}$$
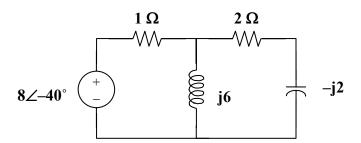
# Chapter 11, Solution 5.

Converting the circuit into the frequency domain, we get:



$$I_{1\Omega} = \frac{8\angle -40^{\circ}}{1 + \frac{j6(2 - j2)}{j6 + 2 - j2}} = 1.6828\angle -25.38^{\circ}$$


$$P_{1\Omega} = \frac{1.6828^2}{2} 1 = \underline{1.4159 \,\mathrm{W}}$$

$$P_{3H} = P_{0.25F} = \underline{\mathbf{0}}$$

$$\left|I_{2\Omega}\right| = \left|\frac{j6}{j6 + 2 - j2}1.6828 \angle - 25.38^{\circ}\right| = 2.258$$

$$P_{2\Omega} = \frac{2.258^2}{2} 2 = \underline{5.097 \, W}$$

## Chapter 11, Solution 6.

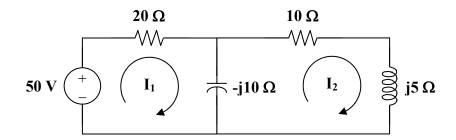

For mesh 1,

$$(4+j2)\mathbf{I}_{1} - j2(4\angle 60^{\circ}) + 4\mathbf{V}_{o} = 0$$
 (1)

$$\mathbf{V}_{0} = 2(4\angle 60^{\circ} - \mathbf{I}_{2}) \tag{2}$$

For mesh 2,

$$(2-j)\mathbf{I}_2 - 2(4\angle 60^\circ) - 4\mathbf{V}_0 = 0 \tag{3}$$

Substituting (2) into (3),

$$(2-j)\mathbf{I}_2 - 8\angle 60^\circ - 8(4\angle 60^\circ - \mathbf{I}_2) = 0$$

$$\mathbf{I}_2 = \frac{40 \angle 60^{\circ}}{10 - \mathbf{j}}$$

Hence,

$$\mathbf{V}_{o} = 2 \left( 4 \angle 60^{\circ} - \frac{40 \angle 60^{\circ}}{10 - i} \right) = \frac{-j8 \angle 60^{\circ}}{10 - i}$$


Substituting this into (1),

$$(4+j2)\mathbf{I}_1 = j8\angle 60^\circ + \frac{j32\angle 60^\circ}{10-j} = (j8\angle 60^\circ)\left(\frac{14-j}{10-j}\right)$$

$$\mathbf{I}_1 = \frac{(4\angle 60^\circ)(1+j14)}{21+j8} = 2.498\angle 125.06^\circ$$

$$P_4 = \frac{1}{2} |\mathbf{I}_1|^2 R = \frac{1}{2} (2.498)^2 (4) = \underline{\mathbf{12.48 W}}$$

## Chapter 11, Solution 7.

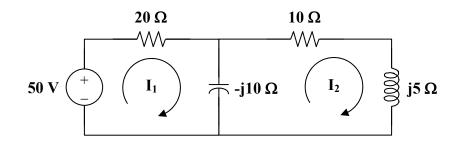

Applying KVL to the left-hand side of the circuit,

$$8 \angle 20^{\circ} = 4 \mathbf{I}_{o} + 0.1 \mathbf{V}_{o} \tag{1}$$

Applying KCL to the right side of the circuit,

$$8\mathbf{I}_{o} + \frac{\mathbf{V}_{1}}{j5} + \frac{\mathbf{V}_{1}}{10 - j5} = 0$$

$$\mathbf{V}_{o} = \frac{10}{10 - \mathrm{j}5} \mathbf{V}_{1} \longrightarrow \mathbf{V}_{1} = \frac{10 - \mathrm{j}5}{10} \mathbf{V}_{o}$$

Hence,

$$8\mathbf{I}_{o} + \frac{10 - j5}{j50}\mathbf{V}_{o} + \frac{\mathbf{V}_{o}}{10} = 0$$

$$\mathbf{I}_{o} = \mathbf{j}0.025\,\mathbf{V}_{o} \tag{2}$$

Substituting (2) into (1),

$$8 \angle 20^{\circ} = 0.1 V_{o} (1 + j)$$


$$\mathbf{V}_{o} = \frac{80 \angle 20^{\circ}}{1+j}$$

$$I_1 = \frac{V_o}{10} = \frac{10}{\sqrt{2}} \angle -25^\circ$$

$$P = \frac{1}{2} |\mathbf{I}_1|^2 R = \left(\frac{1}{2}\right) \left(\frac{100}{2}\right) (10) = \mathbf{250 W}$$
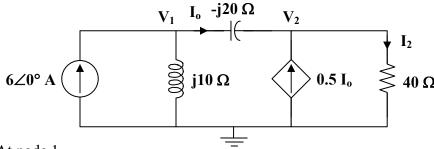
#### Chapter 11, Solution 8.

We apply nodal analysis to the following circuit.



At node 1,

$$6 = \frac{\mathbf{V}_1}{j10} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j20} \ \mathbf{V}_1 = j120 - \mathbf{V}_2$$
 (1)

At node 2,

$$0.5\,\mathbf{I}_{\mathrm{o}} + \mathbf{I}_{\mathrm{o}} = \frac{\mathbf{V}_{2}}{40}$$

$$\mathbf{I}_{o} = \frac{\mathbf{V}_{1} - \mathbf{V}_{2}}{-j20}$$

$$\frac{1.5(\mathbf{V}_1 - \mathbf{V}_2)}{-j20} = \frac{\mathbf{V}_2}{40}$$

$$3\mathbf{V}_1 = (3-\mathbf{j})\mathbf{V}_2 \tag{2}$$

Substituting (1) into (2),

$$j360 - 3V_2 - 3V_2 + jV_2 = 0$$

$$\mathbf{V}_2 = \frac{\mathbf{j}360}{6 - \mathbf{j}} = \frac{360}{37} (-1 + \mathbf{j}6)$$

$$I_2 = \frac{V_2}{40} = \frac{9}{37}(-1 + j6)$$

$$P = \frac{1}{2} |\mathbf{I}_2|^2 R = \frac{1}{2} \left( \frac{9}{\sqrt{37}} \right)^2 (40) = \underline{\mathbf{43.78 W}}$$

# Chapter 11, Solution 9.

$$V_o = \left(1 + \frac{6}{2}\right)V_s = (4)(2) = 8 \text{ V rms}$$

$$P_{10} = \frac{V_o^2}{R} = \frac{64}{10} \text{ mW} = \underline{\textbf{6.4 mW}}$$

The current through the  $2 - k\Omega$  resistor is

$$\frac{V_s}{2k} = 1 \text{ mA}$$

$$P_2 = I^2 R = \underline{2 mW}$$

Similarly,

$$P_6 = I^2 R = 6 \text{ mW}$$

## Chapter 11, Solution 10.

No current flows through each of the resistors. Hence, for each resistor,  $P=\mathbf{0}\ \mathbf{W}$  .

#### Chapter 11, Solution 11.

$$\begin{split} &\omega = 377 \;, \qquad R = 10^4 \;, \qquad C = 200 \times 10^{-9} \\ &\omega RC = (377)(10^4)(200 \times 10^{-9}) = 0.754 \\ &\tan^{-1}(\omega RC) = 37.02^\circ \end{split}$$

$$Z_{ab} = \frac{10k}{\sqrt{1 + (0.754)^2}} \angle -37.02^\circ = 6.375 \angle -37.02^\circ k\Omega$$

$$i(t) = 2\sin(377t + 22^\circ) = 2\cos(377t - 68^\circ) \text{ mA}$$
  
 $I = 2\angle -68^\circ$ 

$$S = I_{rms}^{2} Z_{ab} = \left(\frac{2 \times 10^{-3}}{\sqrt{2}}\right)^{2} (6.375 \angle -37.02^{\circ}) \times 10^{3}$$

$$S = 12.751 \angle -37.02^{\circ} \text{ mVA}$$

$$P = |S| \cos(37.02) = 10.181 \text{ mW}$$

## Chapter 11, Solution 12.


(a) We find  $\mathbf{Z}_{Th}$  using the circuit in Fig. (a).

$$8 \Omega \stackrel{ ext{$\subset$}}{\stackrel{ ext{$\sim$}}{\longleftarrow}} -j2 \Omega$$

$$\mathbf{Z}_{Th} = 8 \parallel -j2 = \frac{(8)(-j2)}{8-j2} = \frac{8}{17}(1-j4) = 0.471 - j1.882$$

$$\boldsymbol{Z}_{L} = \boldsymbol{Z}_{Th}^{*} = \underline{\boldsymbol{0.471 + j1.882 \, \Omega}}$$

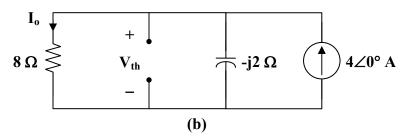We find  $V_{Th}$  using the circuit in Fig. (b).




$$I_o = \frac{-j2}{8-j2} (4\angle 0^\circ)$$

$$V_{Th} = 8I_o = \frac{-j64}{8-j2}$$

$$P_{\text{max}} = \frac{\left| \mathbf{V}_{\text{Th}} \right|^2}{8 R_L} = \frac{\left( \frac{64}{\sqrt{68}} \right)^2}{(8)(0.471)} = \mathbf{\underline{15.99 W}}$$

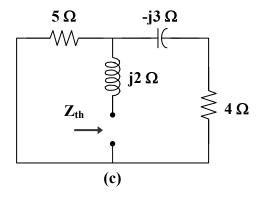(b) We obtain  $\mathbf{Z}_{Th}$  from the circuit in Fig. (c).




$$\mathbf{Z}_{Th} = j2 + 5 \parallel (4 - j3) = j2 + \frac{(5)(4 - j3)}{9 - j3} = 2.5 + j1.167$$

$$\boldsymbol{Z}_{L} = \boldsymbol{Z}_{Th}^{*} = \underline{2.5 - j1.167\,\Omega}$$

## Chapter 11, Solution 13.

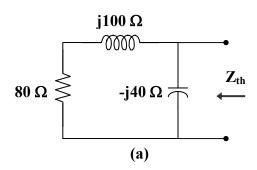
(a) We find  $\mathbf{Z}_{Th}$  at the load terminals using the circuit in Fig. (a).



$$\mathbf{Z}_{Th} = -j40 \parallel (80 + j100) = \frac{(-j40)(80 + j100)}{80 + j60} = 51.2 - j1.6$$

$$\mathbf{Z}_{\mathrm{L}} = \mathbf{Z}_{\mathrm{Th}}^* = \underline{\mathbf{51.2} + \mathbf{j1.6}\,\Omega}$$

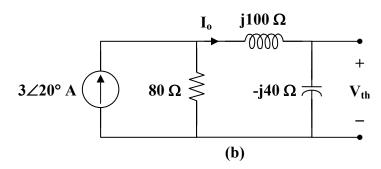(b) We find  $V_{\text{Th}}$  at the load terminals using Fig. (b).




$$\mathbf{I}_{\circ} = \frac{80}{80 + \text{j}100 - \text{j}40} (3 \angle 20^{\circ}) = \frac{(8)(3 \angle 20^{\circ})}{8 + \text{j}6}$$

$$\mathbf{V}_{Th} = -j40 \, \mathbf{I}_{o} = \frac{(-j40)(24 \angle 20^{\circ})}{8 + j6}$$

$$P_{\text{max}} = \frac{\left| \mathbf{V}_{\text{Th}} \right|^2}{8R_L} = \frac{\left( \frac{40}{10} \cdot 24 \right)^2}{(8)(51.2)} = \mathbf{22.5 W}$$

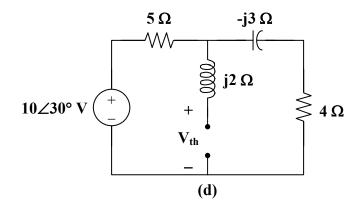
From Fig.(d), we obtain  $V_{Th}$  using the voltage division principle.



$$\mathbf{V}_{\text{Th}} = \left(\frac{4 - j3}{9 - j3}\right) (10 \angle 30^{\circ}) = \left(\frac{4 - j3}{3 - j}\right) \left(\frac{10}{3} \angle 30^{\circ}\right)$$

$$P_{\text{max}} = \frac{\left| \mathbf{V}_{\text{Th}} \right|^2}{8R_L} = \frac{\left( \frac{5}{\sqrt{10}} \cdot \frac{10}{3} \right)^2}{(8)(2.5)} = \mathbf{1.389 W}$$

#### Chapter 11, Solution 14.

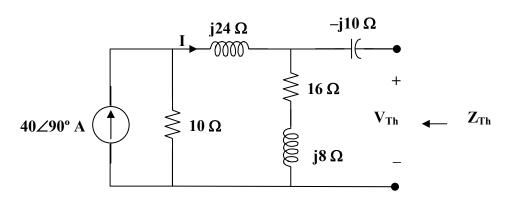


$$\begin{split} Z_{Th} &= -j10 + \frac{(10+j24)(16+j8)}{10+j24+16+j8} = -j10 + 8.245 + j7.7 = 8.245 - j2.3\Omega \\ Z &= Z_{Th}^* = \underline{8.245+j2.3\Omega} \end{split}$$

$$V_{Th} = I(16 + j8) = \frac{10}{10 + j24 + 16 + j8} j40(16 + j8)$$
$$= 173.55 \angle 65.66^{\circ} = 71.53 + j158.12 \text{ V}$$

$$P_{\text{max}} = \left| I_{\text{rms}}^2 \right| 8.245 = \frac{\frac{\left| V_{\text{Th}}^2 \right|}{\sqrt{2}^2}}{(2x8.245)^2} 8.245 = \underline{456.6 \,\text{W}}$$
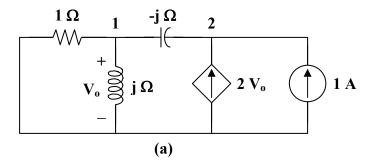
#### Chapter 11, Solution 15.

To find  $\mathbf{Z}_{Th}$ , insert a 1-A current source at the load terminals as shown in Fig. (a).



At node 1,

$$\frac{\mathbf{V}_{o}}{1} + \frac{\mathbf{V}_{o}}{\mathbf{j}} = \frac{\mathbf{V}_{2} - \mathbf{V}_{o}}{-\mathbf{j}} \longrightarrow \mathbf{V}_{o} = \mathbf{j} \mathbf{V}_{2}$$
 (1)

At node 2,

$$1 + 2\mathbf{V}_{o} = \frac{\mathbf{V}_{2} - \mathbf{V}_{o}}{\mathbf{j}} \longrightarrow 1 = \mathbf{j}\mathbf{V}_{2} - (2 + \mathbf{j})\mathbf{V}_{o}$$
 (2)

Substituting (1) into (2),


$$1 = j \mathbf{V}_2 - (2 + j)(j) \mathbf{V}_2 = (1 - j) \mathbf{V}_2$$

$$\mathbf{V}_2 = \frac{1}{1-\mathbf{j}}$$

$$\mathbf{V}_{\text{Th}} = \frac{\mathbf{V}_2}{1} = \frac{1+j}{2} = 0.5 + j0.5$$

$$\boldsymbol{Z}_{L} = \boldsymbol{Z}_{Th}^{*} = \underline{\boldsymbol{0.5 - j0.5\,\Omega}}$$


We now obtain  $V_{Th}$  from Fig. (b).

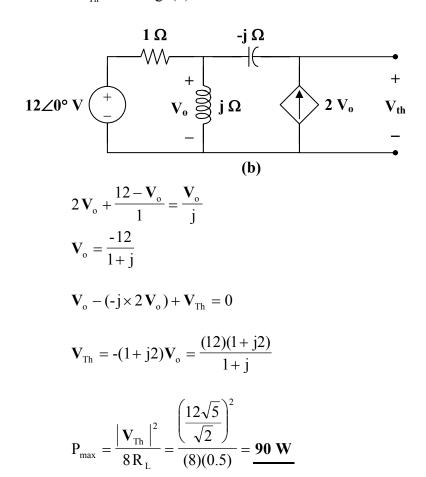
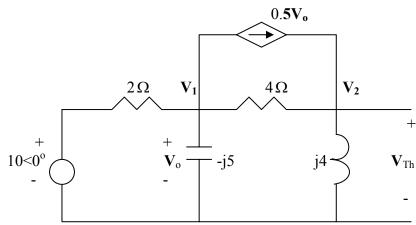
## Chapter 11, Solution 16.

$$\omega = 4$$
, 1H  $\longrightarrow j\omega L = j4$ ,  $1/20$ F  $\longrightarrow \frac{1}{j\omega C} = \frac{1}{j4x1/20} = -j5$ 

We find the Thevenin equivalent at the terminals of  $Z_L$ . To find  $V_{Th}$ , we use the circuit shown below.



At node 1,

$$\frac{10 - V_1}{2} = \frac{V_1}{-j5} + 0.25V_1 + \frac{V_1 - V_2}{4} \longrightarrow 5 = V_1(1 + j0.2) - 0.25V_2$$
 (1)


At node 2,

$$\frac{V_1 - V_2}{4} + 0.25V_1 = \frac{V_2}{j4} \longrightarrow 0 = 0.5V_1 + V_2(-0.25 + j0.25)$$
 (2)

Solving (1) and (2) leads to  $V_{Th} = V_2 = 6.1947 + j7.0796 = \underline{9.4072} \angle 48.81^{\circ}$ 
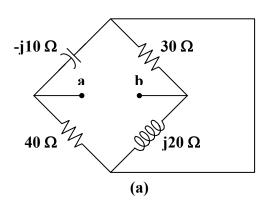
#### Chapter 11, Solution 17.

We find  $R_{Th}$  at terminals a-b following Fig. (a).




$$\mathbf{Z}_{Th} = 30 \parallel j20 + 40 \parallel (-j10) = \frac{(30)(j20)}{30 + j20} + \frac{(40)(-j10)}{40 - j10}$$

$$\mathbf{Z}_{Th} = 9.23 + j13.85 + 2.353 - j9.41$$

$$\mathbf{Z}_{Th} = 11.583 + j4.44 \,\Omega$$

$$\boldsymbol{Z}_{\mathrm{L}} = \boldsymbol{Z}_{\mathrm{Th}}^* = \underline{11.583 - j4.44\,\Omega}$$

We obtain  $V_{Th}$  from Fig. (b).

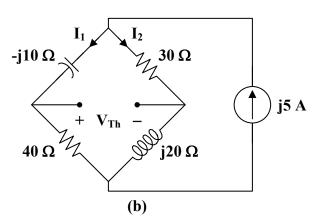

Using current division,

$$\mathbf{I}_1 = \frac{30 + j20}{70 + j10}(j5) = -1.1 + j2.3$$


$$I_2 = \frac{40 - j10}{70 + j10}(j5) = 1.1 + j2.7$$

$$\mathbf{V}_{Th} = 30\,\mathbf{I}_2 + j10\,\mathbf{I}_1 = 10 + j70$$

$$P_{\text{max}} = \frac{\left| \mathbf{V}_{\text{Th}} \right|^2}{8R_L} = \frac{5000}{(8)(11.583)} = \mathbf{53.96 W}$$
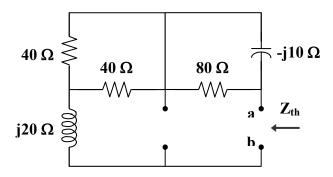
#### Chapter 11, Solution 18.

We find  $\mathbf{Z}_{Th}$  at terminals a-b as shown in the figure below.



$$\mathbf{Z}_{Th} = j20 + 40 \parallel 40 + 80 \parallel (-j10) = j20 + 20 + \frac{(80)(-j10)}{80 - j10}$$

$$\mathbf{Z}_{Th} = 21.23 + j10.154$$

$$\mathbf{Z}_{\mathrm{L}} = \mathbf{Z}_{\mathrm{Th}}^* = \underline{\mathbf{21.23 - j10.15\,\Omega}}$$

## Chapter 11, Solution 19.

At the load terminals,

$$\mathbf{Z}_{Th} = -j2 + 6 \parallel (3+j) = -j2 + \frac{(6)(3+j)}{9+j}$$

$$\mathbf{Z}_{Th} = 2.049 - j1.561$$

$$R_L = \left| \mathbf{Z}_{Th} \right| = 2.576 \,\Omega$$

To get 
$$V_{Th}$$
, let  $Z = 6 \parallel (3 + j) = 2.049 + j0.439$ .

By transforming the current sources, we obtain


$$V_{Th} = (4\angle 0^{\circ}) \mathbf{Z} = 8.196 + j1.756$$

$$P_{\text{max}} = \frac{\left| \mathbf{V}_{\text{Th}} \right|^2}{8R_{\text{I}}} = \frac{70.258}{20.608} = \mathbf{3.409 W}$$

### Chapter 11, Solution 20.

Combine j20  $\Omega$  and -j10  $\Omega$  to get j20 || -j10 = -j20

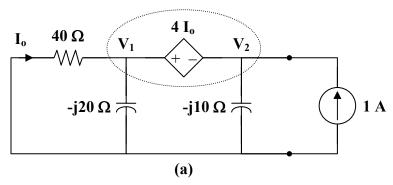To find  $\mathbf{Z}_{Th}$ , insert a 1-A current source at the terminals of  $R_L$ , as shown in Fig. (a).



At the supernode,

$$1 = \frac{\mathbf{V}_1}{40} + \frac{\mathbf{V}_1}{-j20} + \frac{\mathbf{V}_2}{-j10}$$

$$40 = (1 + j2)\mathbf{V}_1 + j4\mathbf{V}_2 \tag{1}$$

Also,  $\mathbf{V}_1 = \mathbf{V}_2 + 4\mathbf{I}_o$ , where  $\mathbf{I}_o = \frac{-\mathbf{V}_1}{40}$ 

$$1.1\mathbf{V}_1 = \mathbf{V}_2 \longrightarrow \mathbf{V}_1 = \frac{\mathbf{V}_2}{1.1}$$
 (2)

Substituting (2) into (1),


$$40 = (1+j2)\left(\frac{\mathbf{V}_2}{1.1}\right) + j4\,\mathbf{V}_2$$

$$\mathbf{V}_{2} = \frac{44}{1 + j6.4}$$

$$\mathbf{Z}_{Th} = \frac{\mathbf{V}_{2}}{1} = 1.05 - j6.71\,\Omega$$

$$\mathbf{R}_{L} = \left|\mathbf{Z}_{Th}\right| = \mathbf{6.792}\,\Omega$$

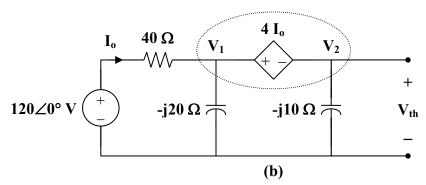To find  $V_{Th}$ , consider the circuit in Fig. (b).



At the supernode,

$$\frac{120 - \mathbf{V}_1}{40} = \frac{\mathbf{V}_1}{-j20} + \frac{\mathbf{V}_2}{-j10}$$

$$120 = (1+j2)\mathbf{V}_1 + j4\mathbf{V}_2 \tag{3}$$

Also,  $\mathbf{V}_1 = \mathbf{V}_2 + 4\mathbf{I}_o$ , where  $\mathbf{I}_o = \frac{120 - \mathbf{V}_1}{40}$ 

$$\mathbf{V}_{1} = \frac{\mathbf{V}_{2} + 12}{1.1} \tag{4}$$

Substituting (4) into (3),


$$109.09 - \mathrm{j}21.82 = (0.9091 + \mathrm{j}5.818)\,\mathbf{V}_2$$

$$\mathbf{V}_{\text{Th}} = \mathbf{V}_2 = \frac{109.09 - \text{j}21.82}{0.9091 + \text{j}5.818} = 18.893 \angle -92.43^{\circ}$$

$$P_{\text{max}} = \frac{\left| \mathbf{V}_{\text{Th}} \right|^2}{8R_L} = \frac{(18.893)^2}{(8)(6.792)} = \underline{\mathbf{6.569 W}}$$
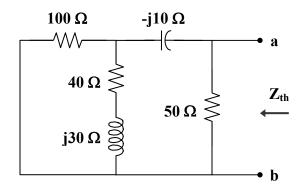
#### Chapter 11, Solution 21.

We find  $\mathbf{Z}_{Th}$  at terminals a-b, as shown in the figure below.



$$\mathbf{Z}_{Th} = 50 \| [-j10 + 100 \| (40 + j30)]$$

where 
$$100 \parallel (40 + j30) = \frac{(100)(40 + j30)}{140 + j30} = 31.707 + j14.634$$

$$\mathbf{Z}_{Th} = 50 \parallel (31.707 + j4.634) = \frac{(50)(31.707 + j4.634)}{81.707 + j4.634}$$

$$\mathbf{Z}_{Th} = 19.5 + j1.73$$

$$R_{_{\mathrm{L}}}=\left|\,\mathbf{Z}_{_{Th}}\,\,\right|=19.58\,\Omega$$

#### Chapter 11, Solution 22.

$$i(t) = 4\sin t, \qquad 0 < t < \pi$$

$$I_{rms}^{2} = \frac{1}{\pi} \int_{0}^{\pi} 16 \sin^{2} t dt = \frac{16}{\pi} \left( \frac{t}{2} - \frac{\sin 2t}{4} \right) \Big|_{0}^{\pi} = \frac{16}{\pi} (\frac{\pi}{2} - 0) = 8$$

$$I_{rms} = \sqrt{8} = \underline{2.828 \text{ A}}$$

# Chapter 11, Solution 23.

$$v(t) = \begin{cases} 15, & 0 < t < 2 \\ 5, & 2 < t < 6 \end{cases}$$

$$V_{rms}^{2} = \frac{1}{6} \left[ \int_{0}^{2} 15^{2} dt + \int_{2}^{6} 5^{2} dt \right] = \frac{550}{6}$$

$$V_{rms} = \underline{9.574 V}$$

# Chapter 11, Solution 24.

T = 2, 
$$v(t) = \begin{cases} 5, & 0 < t < 1 \\ -5, & 1 < t < 2 \end{cases}$$
$$V_{rms}^{2} = \frac{1}{2} \left[ \int_{0}^{1} 5^{2} dt + \int_{1}^{2} (-5)^{2} dt \right] = \frac{25}{2} [1+1] = 25$$
$$V_{rms} = \underline{5 V}$$

# Chapter 11, Solution 25.

$$f_{rms}^{2} = \frac{1}{T} \int_{0}^{T} f^{2}(t) dt = \frac{1}{3} \left[ \int_{0}^{1} (-4)^{2} dt + \int_{1}^{2} 0 dt + \int_{2}^{3} 4^{2} dt \right]$$
$$= \frac{1}{3} [16 + 0 + 16] = \frac{32}{3}$$

$$f_{rms} = \sqrt{\frac{32}{3}} = \underline{3.266}$$

# Chapter 11, Solution 26.

$$T = 4, v(t) = \begin{cases} 5 & 0 < t < 2 \\ 10 & 2 < t < 4 \end{cases}$$

$$V_{rms}^{2} = \frac{1}{4} \left[ \int_{0}^{2} 5^{2} dt + \int_{2}^{4} (10)^{2} dt \right] = \frac{1}{4} [50 + 200] = 62.5$$

$$V_{rms} = \underline{\textbf{7.906 V}}$$

## Chapter 11, Solution 27.

T = 5, 
$$i(t) = t$$
,  $0 < t < 5$ 

$$I_{rms}^2 = \frac{1}{5} \int_0^5 t^2 dt = \frac{1}{5} \cdot \frac{t^3}{3} \Big|_0^5 = \frac{125}{15} = 8.333$$

$$I_{rms} = \mathbf{2.887 A}$$

# Chapter 11, Solution 28.

$$V_{rms}^{2} = \frac{1}{5} \left[ \int_{0}^{2} (4t)^{2} dt + \int_{2}^{5} 0^{2} dt \right]$$

$$V_{rms}^{2} = \frac{1}{5} \cdot \frac{16t^{3}}{3} \Big|_{0}^{2} = \frac{16}{15} (8) = 8.533$$

$$V_{rms} = \underline{2.92 V}$$

$$P = \frac{V_{rms}^{2}}{R} = \frac{8.533}{2} = \underline{4.267 W}$$

#### Chapter 11, Solution 29.

$$\begin{split} T &= 20\,, \qquad i(t) = \begin{cases} 20 - 2t & 5 < t < 15 \\ -40 + 2t & 15 < t < 25 \end{cases} \\ I_{eff}^2 &= \frac{1}{20} \bigg[ \int_5^{15} (20 - 2t)^2 \ dt + \int_{15}^{25} (-40 + 2t)^2 \ dt \bigg] \\ I_{eff}^2 &= \frac{1}{5} \bigg[ \int_5^{15} (100 - 20t + t^2) \ dt + \int_{15}^{25} (t^2 - 40t + 400) \ dt \bigg] \\ I_{eff}^2 &= \frac{1}{5} \bigg[ \bigg( 100t - 10t^2 + \frac{t^3}{3} \bigg) \bigg]_5^{15} + \bigg( \frac{t^3}{3} - 20t^2 + 400t \bigg) \bigg]_{15}^{25} \bigg] \\ I_{eff}^2 &= \frac{1}{5} [83.33 + 83.33] = 33.332 \\ I_{eff} &= \frac{5.773 \ A}{4} \\ P &= I_{eff}^2 R = 400 \ W \end{split}$$

## Chapter 11, Solution 30.

$$v(t) = \begin{cases} t & 0 < t < 2 \\ -1 & 2 < t < 4 \end{cases}$$

$$V_{rms}^{2} = \frac{1}{4} \left[ \int_{0}^{2} t^{2} dt + \int_{2}^{4} (-1)^{2} dt \right] = \frac{1}{4} \left[ \frac{8}{3} + 2 \right] = 1.1667$$

$$V_{rms} = \underline{1.08 \text{ V}}$$

#### Chapter 11, Solution 31.

$$V^{2}_{rms} = \frac{1}{2} \int_{0}^{2} v(t)dt = \frac{1}{2} \left[ \int_{0}^{1} (2t)^{2} dt + \int_{1}^{2} (-4)^{2} dt \right] = \frac{1}{2} \left[ \frac{4}{3} + 16 \right] = 8.6667$$

$$V_{rms} = 2.944 \text{ V}$$

## Chapter 11, Solution 32.

$$I_{rms}^2 = \frac{1}{2} \left[ \int_0^t (10t^2)^2 dt + \int_1^2 0 dt \right]$$

$$I_{rms}^2 = 50 \int_0^1 t^4 dt = 50 \cdot \frac{t^5}{5} \Big|_0^1 = 10$$

$$I_{rms} = 3.162 A$$

## Chapter 11, Solution 33.

$$i(t) = \begin{cases} 10 & 0 < t < 1 \\ 20 - 10t & 1 < t < 2 \\ 0 & 2 < t < 3 \end{cases}$$

$$I_{rms}^{2} = \frac{1}{3} \left[ \int_{0}^{1} 10^{2} dt + \int_{1}^{2} (20 - 10t)^{2} dt + 0 \right]$$

$$3\,I_{rms}^2 = 100 + 100 \int_1^2 \left(4 - 4t + t^2\right) \, dt = 100 + (100)(1/3) = 133.33$$

$$I_{rms} = \sqrt{\frac{133.33}{3}} = 6.667 \text{ A}$$

# Chapter 11, Solution 34.

$$f_{rms}^{2} = \frac{1}{T} \int_{0}^{T} f^{2}(t) dt = \frac{1}{3} \left[ \int_{0}^{2} (3t)^{2} dt + \int_{2}^{3} 6^{2} dt \right]$$
$$= \frac{1}{3} \left[ \frac{9t^{3}}{3} \Big|_{0}^{2} + 36 \right] = 20$$
$$f_{rms} = \sqrt{20} = \underline{4.472}$$

## Chapter 11, Solution 35.

$$\begin{split} V_{rms}^2 &= \frac{1}{6} \bigg[ \int_0^1 \! 10^2 \ dt + \int_1^2 \! 20^2 \ dt + \int_2^4 \! 30^2 \ dt + \int_4^5 \! 20^2 \ dt + \int_5^6 \! 10^2 \ dt \bigg] \\ V_{rms}^2 &= \frac{1}{6} \big[ 100 + 400 + 1800 + 400 + 100 \big] = 466.67 \\ V_{rms} &= \underline{\textbf{21.6 V}} \end{split}$$

## Chapter 11, Solution 36.

(a) 
$$I_{rms} = \underline{10 \text{ A}}$$
  
(b)  $V^2_{rms} = 4^2 + \left(\frac{3}{\sqrt{2}}\right)^2 \longrightarrow V_{rms} = \sqrt{16 + \frac{9}{2}} = \underline{4.528 \text{ V}}$  (checked)  
(c)  $I_{rms} = \sqrt{64 + \frac{36}{2}} = \underline{9.055 \text{ A}}$   
(d)  $V_{rms} = \sqrt{\frac{25}{2} + \frac{16}{2}} = \underline{4.528 \text{ V}}$ 

#### Chapter 11, Solution 37.

$$i = i_1 + i_2 + i_3 = 8 + 4\sin(t + 10^\circ) + 6\cos(2t + 30^\circ)$$

$$I_{rms} = \sqrt{I^2_{1rms} + I^2_{2rms} + I^2_{3rms}} = \sqrt{64 + \frac{16}{2} + \frac{36}{2}} = \sqrt{90} = 9.487 \text{ A}$$

#### Chapter 11, Solution 38.

0.5 H 
$$\longrightarrow$$
  $j\omega L = j(2\pi)(50)(0.5) = j157.08$   
 $\mathbf{Z} = R + jX_T = 30 + j157.08$ 

$$\mathbf{S} = \frac{\left|\mathbf{V}\right|^2}{\mathbf{Z}^*} = \frac{(210)^2}{30 - \text{j}157.08}$$

Apparent power = 
$$|S| = \frac{(210)^2}{160} = \frac{275.6 \text{ VA}}{160}$$

$$pf = cos\theta = cos \left(tan^{-1} \left(\frac{157.08}{36}\right)\right) = cos(79.19^{\circ})$$

$$pf = 0.1876 \quad (lagging)$$

### Chapter 11, Solution 39.

$$\mathbf{Z}_{\mathrm{T}} = \mathrm{j}4 \parallel (12 - \mathrm{j}8) = \frac{(\mathrm{j}4)(12 - \mathrm{j}8)}{12 - \mathrm{j}4}$$

$$\mathbf{Z}_{\mathrm{T}} = 0.4(3 + \mathrm{j}11) = 4.56 \angle 74.74^{\circ}$$

$$pf = cos(74.74^{\circ}) = \underline{\mathbf{0.2631}}$$

#### Chapter 11, Solution 40.

At node 1,

$$\frac{120\angle 30^{0} - V_{1}}{20} = \frac{V_{1}}{j30} + \frac{V_{1} - V_{2}}{50} \longrightarrow$$

$$103.92 + j60 = V_1(1.4 - j0.6667) - 0.4V_2$$
 (1)

At node 2,

$$\frac{V_1 - V_2}{50} = \frac{V_2}{10} + \frac{V_2}{-j40} \longrightarrow 0 = -V_1 + (6 + j1.25)V_2$$
 (2)

Solving (1) and (2) leads to

$$V_1 = 45.045 + j66.935$$
,  $V_2 = 9.423 + j9.193$ 

(a) 
$$P_{j30\Omega} = 0 = P_{-j40\Omega}$$

$$P_{10\Omega} = \frac{V_{rms}^2}{R} = \frac{1}{2} \frac{|V_2|^2}{R} = 173.3/20 = \underline{8.665 \text{ W}}$$

$$P_{50\Omega} = \frac{1}{2} \frac{|V_1 - V_2|^2}{R} = 4603.1/100 = \underline{46.03 \text{ W}}$$

$$P_{20\Omega} = \frac{1}{2} \frac{|120\angle 30^o - V_1|^2}{R} = 3514/40 = \underline{87.86 \text{ W}}$$

(b) 
$$I = \frac{120 \angle 30^{\circ} - V_1}{20} = 2.944 - j0.3467, \quad V_s = 120 \angle 30^{\circ} = 103.92 + j60$$

$$\overline{S} = \frac{1}{2} V_s I^{\bullet} = 142.5 - j106.3, \quad S = |\overline{S}| = \underline{177.8 \text{ VA}}$$

(c) 
$$pf = 142.5/177.8 = 0.8015$$
 (leading).

# Chapter 11, Solution 41.

(a) 
$$-j2 \parallel (j5-j2) = -j2 \parallel -j3 = \frac{(-j2)(-j3)}{j} = -j6$$

$$\mathbf{Z}_{T} = 4 - j6 = 7.211 \angle -56.31^{\circ}$$

$$pf = \cos(-56.31^{\circ}) = \mathbf{0.5547} \quad \text{(leading)}$$
(b)  $j2 \parallel (4+j) = \frac{(j2)(4+j)}{4+j3} = 0.64 + j1.52$ 

$$\mathbf{Z} = 1 \parallel (0.64 + j1.52 - j) = \frac{0.64 + j0.44}{1.64 + j0.44} = 0.4793 \angle 21.5^{\circ}$$

$$pf = \cos(21.5^{\circ}) = \mathbf{0.9304} \quad \text{(lagging)}$$

## Chapter 11, Solution 42.

$$pf = 0.86 = cos\theta \longrightarrow \theta = 30.683^{\circ}$$

$$Q = S \sin \theta \longrightarrow S = \frac{Q}{\sin \theta} = \frac{5}{\sin(30.683^\circ)} = 9.798 \text{ kVA}$$

$$S = VI^* \longrightarrow I^* = \frac{S}{V} = \frac{9.798 \times 10^3 \angle 30.683^\circ}{220} = 44.536 \angle 30.683^\circ$$

Peak current = 
$$\sqrt{2} \times 44.536 = 62.98 \text{ A}$$

Apparent power = 
$$S = 9.798 \text{ kVA}$$

#### Chapter 11, Solution 43.

(a) 
$$V_{rms} = \sqrt{V_{1rms}^2 + V_{2rms}^2 + V_{3rms}^2} = \sqrt{25 + \frac{9}{2} + \frac{1}{2}} = \sqrt{30} = \underline{5.477 \text{ V}}$$

(b) 
$$P = \frac{V^2_{rms}}{R} = 30/10 = \underline{3 \text{ W}}$$

#### Chapter 11, Solution 44.

$$pf = 0.65 = \cos \theta \longrightarrow \theta = 49.46^{\circ}$$

$$\overline{S} = S(\cos\theta + j\sin\theta) = 50(0.65 + j0.7599) = 32.5 + j38 \text{ kVA}$$

Thus,

Average power = 32.5 kW, Reactive power = 38 kVAR

#### Chapter 11, Solution 45.

(a) 
$$V^2_{rms} = 20^2 + \frac{60^2}{2} = 2200 \longrightarrow V_{rms} = \underline{46.9 \text{ V}}$$

$$I_{rms} = \sqrt{1^2 + \frac{0.5^2}{2}} = \sqrt{1.125} = \underline{1.061A}$$

(b) 
$$P = V_{rms} I_{rms} = \underline{49.74 \text{ W}}$$

## Chapter 11, Solution 46.

(a) 
$$\mathbf{S} = \mathbf{V} \mathbf{I}^* = (220 \angle 30^\circ)(0.5 \angle -60^\circ) = 110 \angle -30^\circ$$
  
 $\mathbf{S} = \mathbf{95.26 - \mathbf{j}55 \ VA}$   
Apparent power = 110 VA

Real power = 95.26 W

Reactive power = 55 VAR

pf is **leading** because current leads voltage

(b) 
$$S = VI^* = (250 \angle -10^\circ)(6.2 \angle 25^\circ) = 1550 \angle 15^\circ$$
  
 $S = 1497.2 + j401.2 VA$ 

Apparent power = 1550 VA

Real power = 1497.2 W

Reactive power = 401.2 VAR

pf is <u>lagging</u> because current lags voltage

(c) 
$$\mathbf{S} = \mathbf{VI}^* = (120 \angle 0^\circ)(2.4 \angle 15^\circ) = 288 \angle 15^\circ$$
  
 $\mathbf{S} = \mathbf{278.2 + j74.54 VA}$ 

Apparent power = 288 VA

Real power =  $278.\overline{2}$  W

Reactive power = 74.54 VAR

pf is lagging because current lags voltage

(d) 
$$\mathbf{S} = \mathbf{V} \mathbf{I}^* = (160 \angle 45^\circ)(8.5 \angle -180^\circ) = 1360 \angle -135^\circ$$
  
 $\mathbf{S} = -961.7 - \mathbf{j}961.7 \text{ VA}$ 

Apparent power = 1360 VA

Real power = -961.7 W

Reactive power = -961.7 VAR

pf is **leading** because current leads voltage

## Chapter 11, Solution 47.

(a) 
$$V = 112 \angle 10^{\circ}$$
,  $I = 4 \angle -50^{\circ}$   
 $S = \frac{1}{2}VI^* = 224 \angle 60^{\circ} = \underline{112 + j194 VA}$   
Average power =  $\underline{112 W}$   
Reactive power =  $\underline{194 VAR}$ 

(b) 
$$V = 160 \angle 0^{\circ}, I = 25 \angle 45^{\circ}$$
  
 $S = \frac{1}{2}VI^{*} = 200 \angle -45^{\circ} = \underline{141.42 - j141.42 \ VA}$ 

Average power =  $\frac{141.42 \text{ W}}{-141.42 \text{ VAR}}$ 

(c) 
$$S = \frac{|V|^2}{Z^*} = \frac{(80)^2}{50 \angle -30^\circ} = 128 \angle 30^\circ = \underline{90.51 + j64 \text{ VA}}$$

Average power = 90.51 WReactive power = 64 VAR

(d) 
$$\mathbf{S} = |\mathbf{I}|^2 \mathbf{Z} = (100)(100 \angle 45^\circ) = 7.071 + \mathbf{j}7.071 \text{ kVA}$$

Average power = 7.071 kW

Reactive power = 7.071 kVAR

## Chapter 11, Solution 48.

(a) 
$$S = P - jQ = 269 - j150 \text{ VA}$$

(b) 
$$\operatorname{pf} = \cos \theta = 0.9 \longrightarrow \theta = 25.84^{\circ}$$

$$Q = S \sin \theta \longrightarrow S = \frac{Q}{\sin \theta} = \frac{2000}{\sin(25.84^{\circ})} = 4588.31$$

$$P = S\cos\theta = 4129.48$$

$$S = 4129 - j2000 \; VA$$

(c) 
$$Q = S \sin \theta \longrightarrow \sin \theta = \frac{Q}{S} = \frac{450}{600} = 0.75$$
  
 $\theta = 48.59$ ,  $pf = 0.6614$   
 $P = S \cos \theta = (600)(0.6614) = 396.86$ 

$$S = 396.9 + j450 \text{ VA}$$

(d) 
$$S = \frac{|\mathbf{V}|^2}{|\mathbf{Z}|} = \frac{(220)^2}{40} = 1210$$
  
 $P = S\cos\theta \longrightarrow \cos\theta = \frac{P}{S} = \frac{1000}{1210} = 0.8264$   
 $\theta = 34.26^\circ$   
 $Q = S\sin\theta = 681.25$   
 $S = 1000 + j681.2 \text{ VA}$ 

# Chapter 11, Solution 49.

(a) 
$$\mathbf{S} = 4 + j \frac{4}{0.86} \sin(\cos^{-1}(0.86)) \text{ kVA}$$
  
 $\mathbf{S} = 4 + j2.373 \text{ kVA}$ 

(b) 
$$pf = \frac{P}{S} = \frac{1.6}{2} 0.8 = \cos \theta \longrightarrow \sin \theta = 0.6$$
  
 $S = 1.6 - j2 \sin \theta = 1.6 - j1.2 \text{ kVA}$ 

(c) 
$$\mathbf{S} = \mathbf{V}_{ms} \, \mathbf{I}_{ms}^* = (208 \angle 20^\circ)(6.5 \angle 50^\circ) \, \text{VA}$$
  
 $\mathbf{S} = 1.352 \angle 70^\circ = \mathbf{0.4624} + \mathbf{j1.2705} \, \mathbf{kVA}$ 

(d) 
$$\mathbf{S} = \frac{|\mathbf{V}|^2}{\mathbf{Z}^*} = \frac{(120)^2}{40 - j60} = \frac{14400}{72.11 \angle -56.31^\circ}$$
  
 $\mathbf{S} = 199.7 \angle 56.31^\circ = \mathbf{110.77 + j166.16 VA}$ 

#### Chapter 11, Solution 50.

(a) 
$$\mathbf{S} = P - jQ = 1000 - j\frac{1000}{0.8}\sin(\cos^{-1}(0.8))$$

$$\mathbf{S} = 1000 - j750$$
But,  $\mathbf{S} = \frac{\left|\mathbf{V}_{rms}\right|^2}{\mathbf{Z}^*}$ 

$$\mathbf{Z}^* = \frac{\left|\mathbf{V}_{rms}\right|^2}{\mathbf{S}} = \frac{(220)^2}{1000 - j750} = 30.98 + j23.23$$

$$\mathbf{Z} = \underline{\mathbf{30.98 - j23.23}} \Omega$$

(b) 
$$\mathbf{S} = \left| \mathbf{I}_{\text{rms}} \right|^2 \mathbf{Z}$$

$$\mathbf{Z} = \frac{\mathbf{S}}{\left| \mathbf{I}_{\text{rms}} \right|^2} = \frac{1500 + j2000}{(12)^2} = \underline{\mathbf{10.42 + j13.89 \Omega}}$$

(c) 
$$\mathbf{Z}^* = \frac{|\mathbf{V}_{rms}|^2}{\mathbf{S}} = \frac{|\mathbf{V}|^2}{2\mathbf{S}} = \frac{(120)^2}{(2)(4500\angle 60^\circ)} = 1.6\angle -60^\circ$$
  
 $\mathbf{Z} = 1.6\angle 60^\circ = \mathbf{0.8} + \mathbf{j1.386}\,\Omega$ 

## Chapter 11, Solution 51.

(a) 
$$\mathbf{Z}_{T} = 2 + (10 - j5) || (8 + j6)$$
  
 $\mathbf{Z}_{T} = 2 + \frac{(10 - j5)(8 + j6)}{18 + j} = 2 + \frac{110 + j20}{18 + j}$ 

$$\mathbf{Z}_{\mathrm{T}} = 8.152 + \mathrm{j}0.768 = 8.188 \angle 5.382^{\circ}$$

$$pf = cos(5.382^{\circ}) = 0.9956$$
 (lagging)

(b) 
$$\mathbf{S} = \frac{1}{2} \mathbf{V} \mathbf{I}^* = \frac{\left| \mathbf{V} \right|^2}{2 \mathbf{Z}^*} = \frac{(16)^2}{(2)(8.188 \angle -5.382^\circ)}$$

$$S = 15.63 \angle 5.382^{\circ}$$

$$P = S\cos\theta = 15.56 \text{ W}$$

(c) 
$$Q = S \sin \theta = 1.466 \text{ VAR}$$

(d) 
$$S = |S| = 15.63 \text{ VA}$$

(e) 
$$S = 15.63 \angle 5.382^{\circ} = 15.56 + j1.466 \text{ VA}$$

#### Chapter 11, Solution 52.

$$\begin{split} S_A &= 2000 + j \frac{2000}{0.8} 0.6 = 2000 + j1500 \\ S_B &= 3000 \times 0.4 - j3000 \times 0.9165 = 1200 - j2749 \\ S_C &= 1000 + j500 \\ S &= S_A + S_B + S_C = 4200 - j749 \end{split}$$

(a) 
$$pf = \frac{4200}{\sqrt{4200^2 + 749^2}} = \underline{0.9845 \text{ leading.}}$$

(b) 
$$S = V_{rms}I_{rms}^* \longrightarrow I_{rms}^* = \frac{4200 - j749}{120 \angle 45^\circ} = 35.55 \angle -55.11^\circ$$

$$I_{rms} = 35.55 \angle -55.11^{\circ} A$$
.

#### Chapter 11, Solution 53.

$$S = S_A + S_B + S_C = 4000(0.8-j0.6) + 2400(0.6+j0.8) + 1000 + j500$$
$$= 5640 + j20 = 5640 \angle 0.2^{\circ}$$

(a) 
$$I_{rms}^* = \frac{S_B}{V_{rms}} + \frac{S_A + S_C}{V_{rms}} = \frac{S}{V_{rms}} = \frac{5640 \angle 0.2^{\circ}}{\frac{120 \angle 30^{\circ}}{\sqrt{2}}} = 66.46 \angle -29.8^{\circ}$$

$$I = \sqrt{2}x66.46 \angle 29.88^{\circ} = 93.97 \angle 29.8^{\circ} A$$

(b)  $pf = cos(0.2^\circ) \approx 1.0 lagging$ 

# Chapter 11, Solution 54.

(a) 
$$\mathbf{S} = P - jQ = 1000 - j\frac{1000}{0.8}\sin(\cos^{-1}(0.8))$$

$$\mathbf{S} = 1000 - j750$$

But, 
$$S = \frac{\left| \mathbf{V}_{\text{rms}} \right|^2}{\mathbf{Z}^*}$$

$$\mathbf{Z}^* = \frac{\left|\mathbf{V}_{\text{rms}}\right|^2}{\mathbf{S}} = \frac{(220)^2}{1000 - j750} = 30.98 + j23.23$$

$$Z = \underline{30.98 - j23.23\;\Omega}$$

(b) 
$$\mathbf{S} = \left| \mathbf{I}_{\text{rms}} \right|^2 \mathbf{Z}$$


$$\mathbf{Z} = \frac{\mathbf{S}}{\left|\mathbf{I}_{\text{rms}}\right|^2} = \frac{1500 + j2000}{(12)^2} = \frac{\mathbf{10.42 + j13.89 \,\Omega}}{}$$

(c) 
$$\mathbf{Z}^* = \frac{\left|\mathbf{V}_{rms}\right|^2}{\mathbf{S}} = \frac{\left|\mathbf{V}\right|^2}{2\mathbf{S}} = \frac{(120)^2}{(2)(4500\angle 60^\circ)} = 1.6\angle -60^\circ$$

$$Z = 1.6 \angle 60^{\circ} = 0.8 + j1.386 \Omega$$
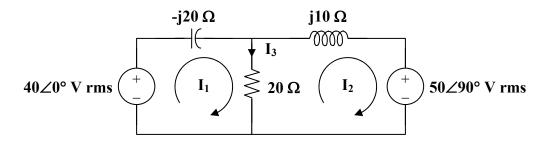
## Chapter 11, Solution 55.

We apply mesh analysis to the following circuit.



For mesh 1, 
$$40 = (20 - j20)I_1 - 20I_2$$
  
 $2 = (1 - j)I_1 - I_2$  (1)

For mesh 2, 
$$-j50 = (20 + j10)I_2 - 20I_1$$
  
 $-j5 = -2I_1 + (2 + j)I_2$  (2)

Putting (1) and (2) in matrix form,

$$\begin{bmatrix} 2 \\ -j5 \end{bmatrix} = \begin{bmatrix} 1-j & -1 \\ -2 & 2+j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Delta = 1 - j$$
,  $\Delta_1 = 4 - j3$ ,  $\Delta_2 = -1 - j5$ 

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{4 - j3}{1 - j} = \frac{1}{2}(7 - j) = 3.535 \angle 8.13^{\circ}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-1 - j5}{1 - i} = 2 - j3 = 3.605 \angle -56.31^\circ$$

$$I_3 = I_1 - I_2 = (3.5 + j0.5) - (2 - j3) = 1.5 + j3.5 = 3.808 \angle 66.8^{\circ}$$

For the 40-V source,

$$S = -V I_1^* = -(40) \left( \frac{1}{2} \cdot (7 - j) \right) = -140 + j20 VA$$

For the capacitor,

$$\mathbf{S} = \left| \mathbf{I}_{1} \right|^{2} \mathbf{Z}_{c} = -\mathbf{j} \mathbf{250} \mathbf{V} \mathbf{A}$$

For the resistor,

$$\mathbf{S} = \left| \mathbf{I}_3 \right|^2 \mathbf{R} = \mathbf{\underline{290 VA}}$$

For the inductor,

$$\mathbf{S} = \left| \mathbf{I}_2 \right|^2 \mathbf{Z}_{L} = \mathbf{j} \mathbf{1} \mathbf{3} \mathbf{0} \mathbf{V} \mathbf{A}$$

For the j50-V source,


$$S = VI_2^* = (j50)(2 + j3) = -150 + j100 VA$$

## Chapter 11, Solution 56.

$$-j2 \parallel 6 = \frac{(6)(-j2)}{6-j2} = 0.6 - j1.8$$

$$3 + i4 + (-i2) \parallel 6 = 3.6 + i2.2$$

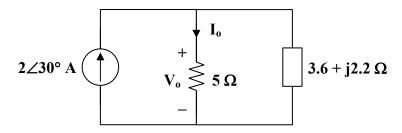The circuit is reduced to that shown below.



$$\mathbf{I}_{o} = \frac{3.6 + j2.2}{8.6 + j2.2} (2 \angle 30^{\circ}) = 0.95 \angle 47.08^{\circ}$$


$$V_0 = 5I_0 = 4.75 \angle 47.08^{\circ}$$

$$\mathbf{S} = \frac{1}{2} \mathbf{V}_{o} \mathbf{I}_{s}^{*} = \frac{1}{2} \cdot (4.75 \angle 47.08^{\circ})(2 \angle -30^{\circ})$$

$$S = 4.75 \angle 17.08^{\circ} = 4.543 + j1.396 \text{ VA}$$

# Chapter 11, Solution 57.

Consider the circuit as shown below.

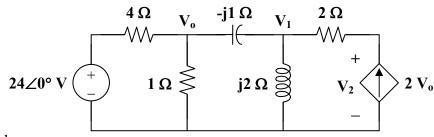

At node o,

$$\frac{24 - \mathbf{V}_{o}}{4} = \frac{\mathbf{V}_{o}}{1} + \frac{\mathbf{V}_{o} - \mathbf{V}_{1}}{-\mathbf{j}}$$

$$24 = (5 + j4)\mathbf{V}_{0} - j4\mathbf{V}_{1} \tag{1}$$

At node 1,  $\frac{\mathbf{V}_{o} - \mathbf{V}_{1}}{-j} + 2\mathbf{V}_{o} = \frac{\mathbf{V}_{1}}{j2}$ 

$$\mathbf{V}_{1} = (2 - \mathbf{j}4)\mathbf{V}_{0} \tag{2}$$

Substituting (2) into (1),

$$24 = (5 + j4 - j8 - 16) \mathbf{V}_{o}$$

$$\mathbf{V}_{o} = \frac{-24}{11 + j4}, \qquad \mathbf{V}_{1} = \frac{(-24)(2 - j4)}{11 + j4}$$

The voltage across the dependent source is

$$V_2 = V_1 + (2)(2V_0) = V_1 + 4V_0$$


$$\mathbf{V}_2 = \frac{-24}{11+j4} \cdot (2-j4+4) = \frac{(-24)(6-j4)}{11+j4}$$

$$\mathbf{S} = \frac{1}{2} \mathbf{V}_2 \mathbf{I}^* = \frac{1}{2} \mathbf{V}_2 (2 \mathbf{V}_0^*)$$

$$\mathbf{S} = \frac{(-24)(6 - j4)}{11 + j4} \cdot \frac{-24}{11 - j4} = \left(\frac{576}{137}\right)(6 - j4)$$

$$S = 25.23 - j16.82 \text{ VA}$$

## Chapter 11, Solution 58.

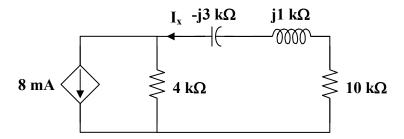

From the left portion of the circuit,

$$I_o = \frac{0.2}{500} = 0.4 \text{ mA}$$

$$20I_{0} = 8 \text{ mA}$$

From the right portion of the circuit,


$$I_x = \frac{4}{4+10+j-j3} (8 \text{ mA}) = \frac{16}{7-j} \text{ mA}$$

$$\mathbf{S} = \left| \mathbf{I}_{x} \right|^{2} \mathbf{R} = \frac{(16 \times 10^{-3})^{2}}{50} \cdot (10 \times 10^{3})$$

$$S = 51.2 \text{ mVA}$$

## Chapter 11, Solution 59.

Consider the circuit below.

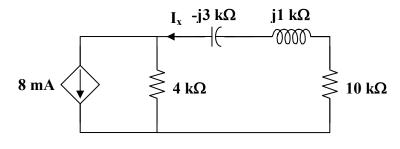

$$4 + \frac{240 - \mathbf{V}_{o}}{50} = \frac{\mathbf{V}_{o}}{-j20} + \frac{\mathbf{V}_{o}}{40 + j30}$$

$$88 = (0.36 + j0.38) \mathbf{V}_{0}$$

$$\mathbf{V}_{0} = \frac{88}{0.36 + \text{j}0.38} = 168.13 \angle -46.55^{\circ}$$

$$I_1 = \frac{V_o}{-i20} = 8.41 \angle 43.45^\circ$$

$$I_2 = \frac{V_o}{40 + i30} = 3.363 \angle -83.42^\circ$$

Reactive power in the inductor is

$$\mathbf{S} = \frac{1}{2} |\mathbf{I}_2|^2 \mathbf{Z}_L = \frac{1}{2} \cdot (3.363)^2 (j30) = \mathbf{\underline{j169.65 \text{ VAR}}}$$

Reactive power in the capacitor is

$$\mathbf{S} = \frac{1}{2} |\mathbf{I}_1|^2 \mathbf{Z}_c = \frac{1}{2} \cdot (8.41)^2 (-j20) = \mathbf{-j707.3 \text{ VAR}}$$

## Chapter 11, Solution 60.

$$S_{1} = 20 + j\frac{20}{0.8}\sin(\cos^{-1}(0.8)) = 20 + j15$$

$$S_{2} = 16 + j\frac{16}{0.9}\sin(\cos^{-1}(0.9)) = 16 + j7.749$$


$$S = S_{1} + S_{2} = 36 + j22.749 = 42.585 \angle 32.29^{\circ}$$
But 
$$S = V_{o} I^{*} = 6V_{o}$$

$$V_{o} = \frac{S}{6} = \underline{7.098} \angle 32.29^{\circ}$$

pf = 
$$\cos(32.29^\circ) = 0.8454$$
 (lagging)

# Chapter 11, Solution 61.

Consider the network shown below.

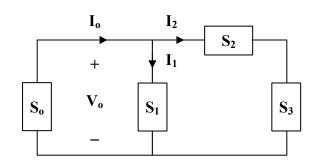

$$\mathbf{S}_2 = 1.2 - j0.8 \text{ kVA}$$

$$\mathbf{S}_3 = 4 + j\frac{4}{0.9}\sin(\cos^{-1}(0.9)) = 4 + j1.937 \text{ kVA}$$

Let 
$$S_4 = S_2 + S_3 = 5.2 + j1.137 \text{ kVA}$$

But 
$$\mathbf{S}_4 = \frac{1}{2} \mathbf{V}_0 \mathbf{I}_2^*$$

$$\mathbf{I}_{2}^{*} = \frac{2\mathbf{S}_{4}}{\mathbf{V}_{o}} = \frac{(2)(5.2 + \mathrm{j}1.137) \times 10^{3}}{100 \angle 90^{\circ}} = 22.74 - \mathrm{j}104$$

$$\mathbf{I}_{2} = 22.74 + \mathrm{j}104$$
Similarly,
$$\mathbf{S}_{1} = 2 - \mathrm{j}\frac{2}{0.707} \sin(\cos^{-1}(0.707)) = 2 - \mathrm{j}2 \text{ kVA}$$
But
$$\mathbf{S}_{1} = \frac{1}{2}\mathbf{V}_{o} \mathbf{I}_{1}^{*}$$

$$\mathbf{I}_{1}^{*} = \frac{2\mathbf{S}_{1}}{\mathbf{V}_{o}} = \frac{(4 - \mathrm{j}4) \times 10^{3}}{\mathrm{j}100} = -40 - \mathrm{j}40$$

$$\mathbf{I}_{1} = -40 + \mathrm{j}40$$

$$\mathbf{I}_{0} = \mathbf{I}_{1} + \mathbf{I}_{2} = -17.26 + \mathrm{j}144 = 145 \angle 96.83^{\circ}$$


$$\mathbf{S}_{0} = \frac{1}{2}\mathbf{V}_{o}\mathbf{I}_{o}^{*}$$

$$\mathbf{S}_{0} = \frac{1}{2} \cdot (100 \angle 90^{\circ})(145 \angle - 96.83^{\circ}) \text{ VA}$$

$$\mathbf{S}_{0} = \frac{7.2 - \mathrm{j}0.862 \text{ kVA}}{2}$$

# Chapter 11, Solution 62.

Consider the circuit below

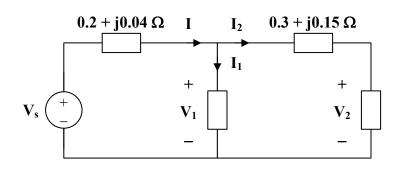

$$\mathbf{S}_2 = 15 - \mathbf{j} \frac{15}{0.8} \sin(\cos^{-1}(0.8)) = 15 - \mathbf{j} 11.25$$
  
 $\mathbf{S}_2 = \mathbf{V}_2 \mathbf{I}_2^*$ 

$$\mathbf{I}_{2}^{*} = \frac{\mathbf{S}_{2}}{\mathbf{V}_{2}} = \frac{15 - \text{j}11.25}{120}$$

$$\mathbf{I}_{2} = 0.125 + j0.09375$$

$$\mathbf{V}_{1} = \mathbf{V}_{2} + \mathbf{I}_{2} (0.3 + j0.15)$$

$$\mathbf{V}_{1} = 120 + (0.125 + j0.09375)(0.3 + j0.15)$$

$$\mathbf{V}_{1} = 120.02 + j0.0469$$

$$\mathbf{S}_1 = 10 + \mathrm{j} \frac{10}{0.9} \sin(\cos^{-1}(0.9)) = 10 + \mathrm{j} 4.843$$

But 
$$\mathbf{S}_1 = \mathbf{V}_1 \mathbf{I}_1^*$$

But

$$\mathbf{I}_{1}^{*} = \frac{\mathbf{S}_{1}}{\mathbf{V}_{1}} = \frac{11.111 \angle 25.84^{\circ}}{120.02 \angle 0.02^{\circ}}$$

$$\begin{split} \mathbf{I}_1 &= 0.093 \angle - 25.82^\circ = 0.0837 - j0.0405 \\ \mathbf{I} &= \mathbf{I}_1 + \mathbf{I}_2 = 0.2087 + j0.053 \\ \mathbf{V}_s &= \mathbf{V}_1 + \mathbf{I}(0.2 + j0.04) \\ \mathbf{V}_s &= (120.02 + j0.0469) + (0.2087 + j0.053)(0.2 + j0.04) \\ \mathbf{V}_s &= 120.06 + j0.0658 \end{split}$$

$$V_s = 120.06 \angle 0.03^{\circ} V$$

## Chapter 11, Solution 63.

Let 
$$\mathbf{S} = \mathbf{S}_1 + \mathbf{S}_2 + \mathbf{S}_3$$
.  
 $\mathbf{S}_1 = 12 - j \frac{12}{0.866} \sin(\cos^{-1}(0.866)) = 12 - j6.929$   
 $\mathbf{S}_2 = 16 + j \frac{16}{0.85} \sin(\cos^{-1}(0.85)) = 16 + j9.916$ 


$$\mathbf{S}_3 = \frac{(20)(0.6)}{\sin(\cos^{-1}(0.6))} + j20 = 15 + j20$$

$$\mathbf{S} = 43 + j22.987 = \frac{1}{2} \mathbf{V} \mathbf{I}_{o}^{*}$$

$$\mathbf{I}_{o}^{*} = \frac{2\mathbf{S}}{\mathbf{V}} = \frac{44 + j22.98}{110}$$

$$I_{o} = 0.4513 \angle - 27.58^{\circ} A$$

#### Chapter 11, Solution 64.

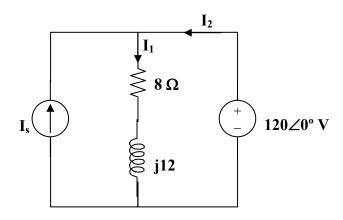

$$I_s + I_2 = I_1 \text{ or } I_s = I_1 - I_2$$

$$I_1 = \frac{120}{8 + j12} = 4.615 - j6.923$$

But, 
$$S = VI_2^* \longrightarrow I_2^* = \frac{S}{V} = \frac{2500 - j400}{120} = 20.83 - j3.333$$
  
or  $I_2 = 20.83 + j3.333$ 

$$I_s = I_1 - I_2 = -16.22 - j10.256 = 19.19 \angle -147.69^{\circ} A.$$

#### Chapter 11, Solution 65.

$$C = 1 \text{ nF} \longrightarrow \frac{1}{j\omega C} = \frac{-j}{10^4 \times 10^{-9}} = -j100 \text{ k}\Omega$$

At the noninverting terminal,

$$\frac{4\angle 0^{\circ} - \mathbf{V}_{o}}{100} = \frac{\mathbf{V}_{o}}{-j100} \longrightarrow \mathbf{V}_{o} = \frac{4}{1+j}$$

$$\mathbf{V}_{o} = \frac{4}{\sqrt{2}} \angle -45^{\circ}$$

$$v_o(t) = \frac{4}{\sqrt{2}}\cos(10^4 t - 45^\circ)$$

$$P = \frac{V_{rms}^{2}}{R} = \left(\frac{4}{\sqrt{2}} \cdot \frac{1}{\sqrt{2}}\right)^{2} \left(\frac{1}{50 \times 10^{3}}\right) W$$

$$P=80~\mu W$$

## Chapter 11, Solution 66.

As an inverter,

$$\mathbf{V}_{o} = \frac{-\mathbf{Z}_{f}}{\mathbf{Z}_{i}} \mathbf{V}_{s} = \frac{-(2+j4)}{4+j3} \cdot (4 \angle 45^{\circ})$$

$$I_o = \frac{V_o}{6 - j2} \text{ mA} = \frac{-(2 + j4)(4 \angle 45^\circ)}{(6 - j2)(4 + j3)} \text{ mA}$$

The power absorbed by the  $6-k\Omega$  resistor is

$$P = \frac{1}{2} |\mathbf{I}_{o}|^{2} R = \frac{1}{2} \cdot \left( \frac{\sqrt{20} \times 4}{\sqrt{40} \times 5} \right)^{2} \times 10^{-6} \times 6 \times 10^{3}$$


$$P = 0.96 \text{ mW}$$

#### Chapter 11, Solution 67.

$$\omega = 2$$
, 3H  $\longrightarrow j\omega L = j6$ , 0.1F  $\longrightarrow \frac{1}{j\omega C} = \frac{1}{j2x0.1} = -j5$ 

$$10/(-j5) = \frac{-j50}{10 - j5} = 2 - j4$$

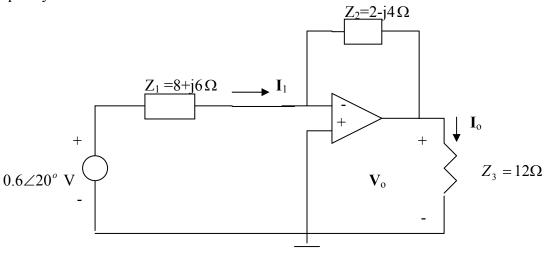The frequency-domain version of the circuit is shown below.



(a) 
$$I_1 = \frac{0.6 \angle 20^\circ - 0}{8 + j6} = \frac{0.5638 + j0.2052}{8 + j6} = 0.06 \angle -16.87^\circ$$

$$S = \frac{1}{2}V_s I_1^* = (0.3 \angle 20^\circ)(0.06 \angle + 16.87^\circ) = \underline{14.4 + j10.8 \text{ mVA}} = \underline{18 \angle 36.86^\circ \text{ mVA}}$$

(b) 
$$V_o = -\frac{Z_2}{Z_1}V_s$$
,  $I_o = \frac{V_o}{Z_3} = -\frac{(2-j4)}{12(8+j6)}(0.6\angle 20^\circ) = 0.0224\angle 99.7^\circ$ 

$$P = \frac{1}{2} |I_o|^2 R = 0.5(0.0224)^2 (12) = \underline{2.904 \text{ mW}}$$

#### Chapter 11, Solution 68.

$$\begin{aligned} \text{Let} \qquad \mathbf{S} &= \mathbf{S}_{\mathrm{R}} + \mathbf{S}_{\mathrm{L}} + \mathbf{S}_{\mathrm{c}} \\ \text{where} \qquad \mathbf{S}_{\mathrm{R}} &= P_{\mathrm{R}} + \mathrm{j} Q_{\mathrm{R}} = \frac{1}{2} \mathrm{I}_{\mathrm{o}}^{2} \, \mathrm{R} + \mathrm{j} 0 \\ \\ \mathbf{S}_{\mathrm{L}} &= P_{\mathrm{L}} + \mathrm{j} Q_{\mathrm{L}} = 0 + \mathrm{j} \frac{1}{2} \mathrm{I}_{\mathrm{o}}^{2} \omega \mathrm{L} \\ \\ \mathbf{S}_{\mathrm{c}} &= P_{\mathrm{c}} + \mathrm{j} Q_{\mathrm{c}} = 0 - \mathrm{j} \frac{1}{2} \mathrm{I}_{\mathrm{o}}^{2} \cdot \frac{1}{\omega \mathrm{C}} \\ \\ \text{Hence,} \qquad \mathbf{S} &= \frac{1}{2} \mathrm{I}_{\mathrm{o}}^{2} \left[ \, \mathbf{R} + \mathrm{j} \! \left( \omega \mathrm{L} - \frac{1}{\omega \mathrm{C}} \right) \right] \end{aligned}$$

#### Chapter 11, Solution 69.

(a) Given that 
$$\mathbf{Z} = 10 + j12$$

$$\tan \theta = \frac{12}{10} \longrightarrow \theta = 50.19^{\circ}$$

$$pf = cos\theta = \mathbf{0.6402}$$

(b) 
$$S = \frac{|V|^2}{2Z^*} = \frac{(120)^2}{(2)(10 - j12)} = 295.12 + j354.09$$

The average power absorbed =  $P = Re(S) = \underline{295.1 \text{ W}}$ 

(c) For unity power factor,  $\theta_1=0^\circ$ , which implies that the reactive power due to the capacitor is  $Q_c=354.09$ 

But 
$$Q_c = \frac{V^2}{2X_c} = \frac{1}{2}\omega C V^2$$

$$C = \frac{2Q_c}{\omega V^2} = \frac{(2)(354.09)}{(2\pi)(60)(120)^2} = \mathbf{130.4 \ \mu F}$$

#### Chapter 11, Solution 70.

$$pf = cos \theta = 0.8 \longrightarrow sin \theta = 0.6$$
  
 $Q = S sin \theta = (880)(0.6) = 528$ 

If the power factor is to be unity, the reactive power due to the capacitor is  $Q_c = Q = 528 \text{ VAR}$ 

But 
$$Q = \frac{V_{rms}^2}{X_c} = \frac{1}{2}\omega C V^2 \longrightarrow C = \frac{2Q_c}{\omega V^2}$$

$$C = \frac{(2)(528)}{(2\pi)(50)(220)^2} = \underline{69.45 \ \mu F}$$

#### Chapter 11, Solution 71.

$$P_1 = Q_1 = 150x0.7071 = 106.065,$$
  $Q_2 = 50,$   $S_2 = \frac{Q_2}{0.6},$   $P_2 = 0.8S = 0.8\frac{50}{0.6} = 66.67$ 

$$\overline{S}_1 = 106.065 + j106.065, \quad \overline{S}_2 = 66.67 - j50$$

$$\overline{S} = \overline{S}_1 + \overline{S}_2 = 172.735 + j56.06 = 181.6 \angle 17.98^\circ, \quad pf = \cos 17.98^\circ = 0.9512$$

$$Q_c = P(\tan \theta_1 - \tan \theta_2) = 172.735(\tan 17.98^\circ - 0) = 56.058$$

$$C = \frac{Q_c}{\omega V_{rms}^2} = \frac{56.058}{2\pi x 60 x 120^2} = \frac{10.33 \,\mu\text{F}}{2}$$

#### Chapter 11, Solution 72.

(a) 
$$\theta_1 = \cos^{-1}(0.76) = 40.54^{\circ}$$
  
 $\theta_2 = \cos^{-1}(0.9) = 25.84^{\circ}$ 

$$Q_{c} = P(\tan \theta_{1} - \tan \theta_{2})$$

$$Q_c = (40)[\tan(40.54^\circ) - \tan(25.84^\circ)] \text{ kVAR}$$

$$Q_c = 14.84 \text{ kVAR}$$

$$C = \frac{Q_c}{\omega V_{rms}^2} = \frac{14840}{(2\pi)(60)(120)^2} = 2.734 \text{ mF}$$

(b) 
$$\theta_1 = 40.54^\circ$$
,  $\theta_2 = 0^\circ$ 

$$Q_c = (40)[\tan(40.54^\circ) - 0] \text{ kVAR} = 34.21 \text{ kVAR}$$

$$C = \frac{Q_c}{\omega V_{rms}^2} \frac{34210}{(2\pi)(60)(120)^2} = \underline{\textbf{6.3 mF}}$$

#### Chapter 11, Solution 73.

(a) 
$$\mathbf{S} = 10 - j15 + j22 = 10 + j7 \text{ kVA}$$
  
 $\mathbf{S} = |\mathbf{S}| = \sqrt{10^2 + 7^2} = \mathbf{12.21 \text{ kVA}}$ 

(b) 
$$\mathbf{S} = \mathbf{VI}^* \longrightarrow \mathbf{I}^* = \frac{\mathbf{S}}{\mathbf{V}} = \frac{10,000 + j7,000}{240}$$
  
 $\mathbf{I} = 41.667 - j29.167 = \mathbf{50.86} \angle -\mathbf{35}^{\circ} \mathbf{A}$ 

(c) 
$$\theta_1 = \tan^{-1} \left( \frac{7}{10} \right) = 35^{\circ}, \qquad \theta_2 = \cos^{-1}(0.96) = 16.26^{\circ}$$

$$Q_c = P_1 [\tan \theta_1 - \tan \theta_2] = 10 [\tan(35^\circ) - \tan(16.26^\circ)]$$
  
 $Q_c = 4.083 \text{ kVAR}$ 

$$C = \frac{Q_c}{\omega V_{rms}^2} = \frac{4083}{(2\pi)(60)(240)^2} = \underline{188.03 \ \mu F}$$

(d) 
$$\mathbf{S}_2 = \mathbf{P}_2 + \mathbf{j}\mathbf{Q}_2$$
,  $\mathbf{P}_2 = \mathbf{P}_1 = 10 \text{ kW}$ 

$$Q_2 = Q_1 - Q_c = 7 - 4.083 = 2.917 \text{ kVAR}$$

$$S_2 = 10 + j2.917 \text{ kVA}$$

But 
$$S_2 = VI_2^*$$

$$\mathbf{I}_{2}^{*} = \frac{\mathbf{S}_{2}}{\mathbf{V}} = \frac{10,000 + j2917}{240}$$

$$I_2 = 41.667 - j12.154 = 43.4 \angle -16.26^{\circ} A$$

## Chapter 11, Solution 74.

(a) 
$$\theta_1 = \cos^{-1}(0.8) = 36.87^{\circ}$$

$$S_1 = \frac{P_1}{\cos \theta_1} = \frac{24}{0.8} = 30 \text{ kVA}$$

$$Q_1 = S_1 \sin \theta_1 = (30)(0.6) = 18 \text{ kVAR}$$

$$\mathbf{S}_1 = 24 + j18 \text{ kVA}$$

$$\theta_2 = \cos^{-1}(0.95) = 18.19^{\circ}$$

$$S_2 = \frac{P_2}{\cos \theta_2} = \frac{40}{0.95} = 42.105 \text{ kVA}$$

$$Q_2 = S_2 \sin \theta_2 = 13.144 \text{ kVAR}$$

$$S_2 = 40 + j13.144 \text{ kVA}$$

$$S = S_1 + S_2 = 64 + j31.144 \text{ kVA}$$

$$\theta = \tan^{-1} \left( \frac{31.144}{64} \right) = 25.95^{\circ}$$

$$pf = \cos\theta = \mathbf{0.8992}$$

(b) 
$$\theta_2 = 25.95^{\circ}, \qquad \theta_1 = 0^{\circ}$$

$$Q_c = P[\tan \theta_2 - \tan \theta_1] = 64[\tan(25.95^\circ) - 0] = 31.144 \text{ kVAR}$$

$$C = \frac{Q_c}{\omega V_{max}^2} = \frac{31,144}{(2\pi)(60)(120)^2} = 5.74 \text{ mF}$$

#### Chapter 11, Solution 75.

(a) 
$$\mathbf{S}_{1} = \frac{\left|\mathbf{V}\right|^{2}}{\mathbf{Z}_{1}^{*}} = \frac{(240)^{2}}{80 + j50} = \frac{5760}{8 + j5} = 517.75 - j323.59 \text{ VA}$$

$$\mathbf{S}_{2} = \frac{(240)^{2}}{120 - j70} = \frac{5760}{12 - j7} = 358.13 + j208.91 \text{ VA}$$

$$\mathbf{S}_{3} = \frac{(240)^{2}}{60} = 960 \text{ VA}$$

$$\mathbf{S} = \mathbf{S}_{1} + \mathbf{S}_{2} + \mathbf{S}_{3} = \underline{\mathbf{1835.88 - j114.68 VA}}$$

(b) 
$$\theta = \tan^{-1} \left( \frac{114.68}{1835.88} \right) = 3.574^{\circ}$$


$$pf = cos\theta = \mathbf{0.998}$$

(c) 
$$Q_c = P[\tan \theta_2 - \tan \theta_1] = 18.35.88[\tan(3.574^\circ) - 0]$$
  
 $Q_c = 114.68 \text{ VAR}$ 

$$C = {Q_c \over \omega V_{rms}^2} = {114.68 \over (2\pi)(50)(240)^2} = {\bf 6.336 \ \mu F}$$
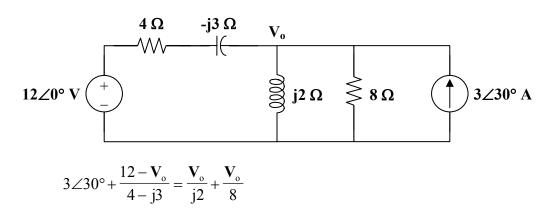
#### Chapter 11, Solution 76.

The wattmeter reads the real power supplied by the current source. Consider the circuit below.



$$\mathbf{V}_{o} = \frac{36.14 + j23.52}{2.28 - j3.04} = 0.7547 + j11.322 = 11.347 \angle 86.19^{\circ}$$

$$\mathbf{S} = \frac{1}{2} \mathbf{V}_{o} \mathbf{I}_{o}^{*} = \frac{1}{2} \cdot (11.347 \angle 86.19^{\circ})(3 \angle -30^{\circ})$$

$$\mathbf{S} = 17.021 \angle 56.19^{\circ}$$

$$\mathbf{P} = \text{Re}(\mathbf{S}) = \mathbf{9.471} \mathbf{W}$$

#### Chapter 11, Solution 77.


The wattmeter measures the power absorbed by the parallel combination of 0.1 F and 150  $\Omega$ .

$$120\cos(2t) \longrightarrow 120 \angle 0^{\circ}, \qquad \omega = 2$$

$$4 \text{ H} \longrightarrow j\omega L = j8$$

$$0.1 \text{ F} \longrightarrow \frac{1}{j\omega C} = -j5$$

Consider the following circuit.

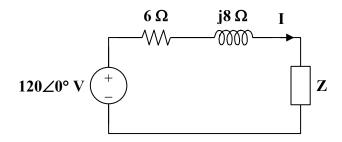

$$\mathbf{Z} = 15 \parallel (-j5) = \frac{(15)(-j5)}{15 - j5} = 1.5 - j4.5$$

$$\mathbf{I} = \frac{120}{(6+j8) + (1.5-j4.5)} = 14.5 \angle -25.02^{\circ}$$

$$\mathbf{S} = \frac{1}{2} \mathbf{V} \mathbf{I}^* = \frac{1}{2} |\mathbf{I}|^2 \mathbf{Z} = \frac{1}{2} \cdot (14.5)^2 (1.5 - j4.5)$$

$$S = 157.69 - j473.06 \text{ VA}$$

The wattmeter reads

$$P = Re(S) = 157.69 W$$

#### Chapter 11, Solution 78.


The wattmeter reads the power absorbed by the element to its right side.

$$2\cos(4t) \longrightarrow 2\angle 0^{\circ}, \qquad \omega = 4$$

$$1 \text{ H} \longrightarrow j\omega L = j4$$

$$\frac{1}{12} \text{ F} \longrightarrow \frac{1}{i\omega C} = -j3$$

Consider the following circuit.

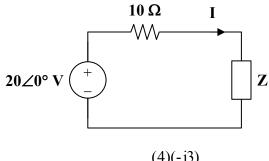

$$\mathbf{Z} = 5 + j4 + 4 \parallel -j3 = 5 + j4 + \frac{(4)(-j3)}{4 - j3}$$

$$\mathbf{Z} = 6.44 + j2.08$$

$$\mathbf{I} = \frac{20}{16.44 + j2.08} = 1.207 \angle -7.21^{\circ}$$

$$\mathbf{S} = \frac{1}{2} |\mathbf{I}|^2 \mathbf{Z} = \frac{1}{2} \cdot (1.207)^2 (6.44 + j2.08)$$

$$P = Re(S) = \underline{4.691 \text{ W}}$$


## Chapter 11, Solution 79.

The wattmeter reads the power supplied by the source and partly absorbed by the 40- $\Omega$  resistor.

$$\omega = 100$$
,

$$10 \, \text{mH} \quad \longrightarrow \quad j100 x 10 x 10^{-3} = j, \quad 500 \mu F \quad \longrightarrow \quad \frac{1}{j \omega C} = \frac{1}{j100 x 500 x 10^{-6}} = -j20$$

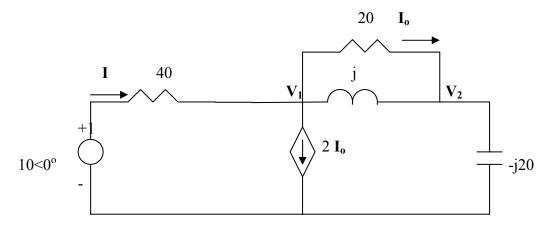The frequency-domain circuit is shown below.



At node 1,

$$\frac{10 - V_1}{40} = 2I_0 + \frac{V_1 - V_2}{j} + \frac{V_1 - V_2}{20} = \frac{3(V_1 - V_2)}{20} + \frac{V_1 - V_2}{j} \longrightarrow 10 = (7 - j40)V_1 + (-6 + j40)V_2$$
(1)

At node 2,

$$\frac{V_1 - V_2}{j} + \frac{V_1 - V_2}{20} = \frac{V_2}{-j20} \longrightarrow 0 = (20 + j)V_1 - (19 + j)V_2$$
 (2)

Solving (1) and (2) yields  $V_1 = 1.5568 - j4.1405$ 

$$I = \frac{10 - V_1}{40} = 0.8443 + j0.4141, \qquad S = \frac{1}{2}VI^{\bullet} = 4.2216 - j2.0703$$

$$P = Re(S) = 4.222 \text{ W}.$$

#### Chapter 11, Solution 80.

(a) 
$$I = \frac{V}{Z} = \frac{110}{6.4} = \underline{17.19 \text{ A}}$$

(b) 
$$\mathbf{S} = \frac{\mathbf{V}^2}{\mathbf{Z}} = \frac{(110)^2}{6.4} = 1890.625$$
  
 $\cos \theta = \text{pf} = 0.825 \longrightarrow \theta = 34.41^\circ$   
 $\mathbf{P} = \mathbf{S} \cos \theta = 1559.76 \cong \mathbf{1.6 \ kW}$ 

## Chapter 11, Solution 81.

kWh consumed = 4017 - 3246 = 771 kWh

The electricity bill is calculated as follows:

- (a) Fixed charge = \$12
- (b) First 100 kWh at \$0.16 per kWh = \$16
- (c) Next 200 kWh at \$0.10 per kWh = \$20
- (d) The remaining energy (771 300) = 471 kWh at \$0.06 per kWh = \$28.26.

Adding (a) to (d) gives **\$76.26** 

#### Chapter 11, Solution 82.

(a) 
$$P_1 = 5,000, \quad Q_1 = 0$$
  
 $P_2 = 30,000x0.82 = 24,600, \quad Q_2 = 30,000\sin(\cos^{-1}0.82) = 17,171$   
 $\overline{S} = \overline{S}_1 + \overline{S}_2 = (P_1 + P_2) + j(Q_1 + Q_2) = 29,600 + j17,171$   
 $S = |\overline{S}| = \underline{34.22 \text{ kV}} \text{A}$ 

(b) 
$$Q = 17.171 \text{ kVAR}$$

(c) 
$$pf = \frac{P}{S} = \frac{29,600}{34,220} = 0.865$$

$$Q_{c} = P(\tan \theta_{1} - \tan \theta_{2})$$

$$= 29,600 \left[ \tan(\cos^{-1} 0.865) - \tan(\cos^{-1} 0.9) \right] = \underline{2833 \text{ VAR}}$$

(d) 
$$C = \frac{Q_c}{\omega V_{rms}^2} = \frac{2833}{2\pi x 60x 240^2} = \underline{130.46 \mu \text{ F}}$$

## Chapter 11, Solution 83.

(a) 
$$\overline{S} = \frac{1}{2}VI^* = \frac{1}{2}(210\angle 60^\circ)(8\angle -25^\circ) = 840\angle 35^\circ$$

$$P = S \cos \theta = 840 \cos 35^\circ = 688.1 \text{ W}$$


- (b) S = 840 VA
- (c)  $Q = S \sin \theta = 840 \sin 35^\circ = 481.8 \text{ VAR}$
- (d)  $pf = P/S = \cos 35^\circ = 0.8191$  (lagging)

## Chapter 11, Solution 84.

- (a) Maximum demand charge =  $2,400 \times 30 = $72,000$ Energy cost =  $$0.04 \times 1,200 \times 10^3 = $48,000$ Total charge = \$120,000
- (b) To obtain \$120,000 from 1,200 MWh will require a flat rate of  $\frac{\$120,000}{1,200 \times 10^3} \text{ per kWh} = \underline{\$0.10 \text{ per kWh}}$

## Chapter 11, Solution 85.

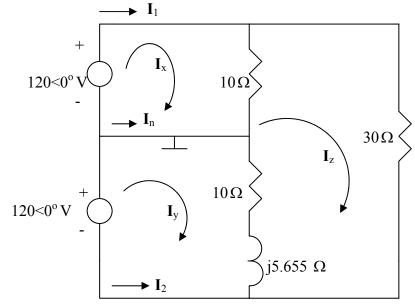(a)  $15 \text{ mH} \longrightarrow j2\pi x 60x 15x 10^{-3} = j5.655$ We apply mesh analysis as shown below.



$$120 = 10 \, \mathbf{I}_{x} - 10 \, \mathbf{I}_{z} \tag{1}$$

For mesh y,

$$120 = (10+j5.655) \mathbf{I}_{v} - (10+j5.655) \mathbf{I}_{z}$$
 (2)

For mesh z,

$$0 = -10 \mathbf{I}_{x} - (10 + j5.655) \mathbf{I}_{y} + (50 + j5.655) \mathbf{I}_{z}$$
 (3)

Solving (1) to (3) gives

$$I_x = 20$$
,  $I_v = 17.09 - j5.142$ ,  $I_z = 8$ 

Thus,

$$I_1 = I_x = 20 \text{ A}$$

$$I_2 = -I_y = -17.09 + j5.142 = 17.85 \angle 163.26^{\circ} A$$

$$I_n = I_v - I_x = -2.091 - j5.142 = 5.907 \angle -119.5^\circ$$
 A

(b) 
$$\overline{S}_1 = \frac{1}{2}(120)I^{\bullet}_x = 60x20 = 1200, \quad \overline{S}_2 = \frac{1}{2}(120)I^{\bullet}_y = 1025.5 - j308.5$$

$$\overline{S} = \overline{S_1} + \overline{S_2} = 2225.5 - j308.5 \text{ VA}$$

(c) 
$$pf = P/S = 2225.5/2246.8 = 0.9905$$

#### Chapter 11, Solution 86.

For maximum power transfer

$$\mathbf{Z}_{L} = \mathbf{Z}_{Th}^{*} \longrightarrow \mathbf{Z}_{i} = \mathbf{Z}_{Th} = \mathbf{Z}_{L}^{*}$$

$$\mathbf{Z}_{L} = R + j\omega L = 75 + j(2\pi)(4.12 \times 10^{6})(4 \times 10^{-6})$$

$$\mathbf{Z}_{\mathrm{L}} = 75 + \mathrm{j}103.55\,\Omega$$

$$Z_{\rm i} = 75 - j103.55\,\Omega$$

#### Chapter 11, Solution 87.

$$\mathbf{Z} = \mathbf{R} \pm \mathbf{j} \mathbf{X}$$

$$V_{R} = IR \longrightarrow R = \frac{V_{R}}{I} = \frac{80}{50 \times 10^{-3}} = 1.6 \text{ k}\Omega$$

$$\left| \mathbf{Z} \right|^2 = R^2 + X^2 \longrightarrow X^2 = \left| \mathbf{Z} \right|^2 - R^2 = (3)^2 - (1.6)^2$$
  
  $X = 2.5377 \text{ k}\Omega$ 

$$\theta = \tan^{-1}\left(\frac{X}{R}\right) = \tan^{-1}\left(\frac{2.5377}{1.6}\right) = 57.77^{\circ}$$

$$pf = cos\theta = \mathbf{0.5333}$$

#### Chapter 11, Solution 88.

(a) 
$$\mathbf{S} = (110)(2\angle 55^{\circ}) = 220\angle 55^{\circ}$$
  
 $P = S\cos\theta = 220\cos(55^{\circ}) = \mathbf{126.2 W}$ 

(b) 
$$S = |S| = 220 \text{ VA}$$

# Chapter 11, Solution 89.

(a) Apparent power = 
$$S = 12 \text{ kVA}$$
  

$$P = S\cos\theta = (12)(0.78) = 9.36 \text{ kW}$$

$$Q = S\sin\theta = 12\sin(\cos^{-1}(0.78)) = 7.51 \text{ kVAR}$$

$$S = P + jQ = 9.36 + j7.51 \text{ kVA}$$

(b) 
$$S = \frac{|V|^2}{Z^*} \longrightarrow Z^* = \frac{|V|^2}{S} = \frac{(210)^2}{(9.36 + j7.51) \times 10^3}$$

$$Z = \underline{34.398 + j27.6 \Omega}$$

#### Chapter 11, Solution 90

Original load:

$$P_1 = 2000 \text{ kW}, \qquad \cos \theta_1 = 0.85 \longrightarrow \theta_1 = 31.79^{\circ}$$
 
$$S_1 = \frac{P_1}{\cos \theta_1} = 2352.94 \text{ kVA}$$
 
$$Q_1 = S_1 \sin \theta_1 = 1239.5 \text{ kVAR}$$

Additional load:

$$P_2 = 300 \text{ kW}, \qquad \cos \theta_2 = 0.8 \longrightarrow \theta_2 = 36.87^{\circ}$$
 
$$S_2 = \frac{P_2}{\cos \theta_2} = 375 \text{ kVA}$$
 
$$Q_2 = S_2 \sin \theta_2 = 225 \text{ kVAR}$$

Total load:

$$S = S_1 + S_2 = (P_1 + P_2) + j(Q_1 + Q_2) = P + jQ$$
  
 $P = 2000 + 300 = 2300 \text{ kW}$   
 $Q = 1239.5 + 225 = 1464.5 \text{ kVAR}$ 

The minimum operating pf for a 2300 kW load and not exceeding the kVA rating of the generator is

$$\cos\theta = \frac{P}{S_1} = \frac{2300}{2352.94} = 0.9775$$

or 
$$\theta = 12.177^{\circ}$$

The maximum load kVAR for this condition is

$$Q_m = S_1 \sin \theta = 2352.94 \sin(12.177^\circ)$$
  
 $Q_m = 496.313 \text{ kVAR}$ 

The capacitor must supply the difference between the total load kVAR (i.e. Q) and the permissible generator kVAR (i.e.  $Q_m$ ). Thus,

$$Q_{c} = Q - Q_{m} = \underline{968.2 \text{ kVAR}}$$

# Chapter 11, Solution 91

$$P = S \cos \theta$$

$$pf = cos \theta = \frac{P}{S} = \frac{2700}{(220)(15)} = \frac{0.8182}{}$$

$$Q = S\sin\theta = 220(15)\sin(35.09^\circ) = 1897.3$$

When the power is raised to unity pf,  $\theta_1 = 0^{\circ}$  and  $Q_c = Q = 1897.3$ 

$$C = \frac{Q_c}{\omega V_{rms}^2} = \frac{1897.3}{(2\pi)(60)(220)^2} = \underline{104 \ \mu F}$$

#### Chapter 11, Solution 92

(a) Apparent power drawn by the motor is

$$S_{m} = \frac{P}{\cos \theta} = \frac{60}{0.75} = 80 \text{ kVA}$$

$$Q_m = \sqrt{S^2 - P^2} = \sqrt{(80)^2 - (60)^2} = 52.915 \text{ kVAR}$$

Total real power

$$P = P_m + P_c + P_L = 60 + 0 + 20 = 80 \text{ kW}$$

Total reactive power

$$Q = Q_m + Q_c + Q_L = 52.915 - 20 + 0 = 32.91 \text{ kVAR}$$

Total apparent power

$$S = \sqrt{P^2 + Q^2} = 86.51 \text{ kVA}$$

(b) 
$$pf = \frac{P}{S} = \frac{80}{86.51} = \underline{0.9248}$$

(c) 
$$I = \frac{S}{V} = \frac{86510}{550} = \underline{157.3 \text{ A}}$$

#### Chapter 11, Solution 93

(a) 
$$P_1 = (5)(0.7457) = 3.7285 \text{ kW}$$

$$S_1 = \frac{P_1}{pf} = \frac{3.7285}{0.8} = 4.661 \text{ kVA}$$

$$Q_1 = S_1 \sin(\cos^{-1}(0.8)) = 2.796 \text{ kVAR}$$

$$S_1 = 3.7285 + j2.796 \text{ kVA}$$

$$P_2 = 1.2 \text{ kW}, \qquad Q_2 = 0 \text{ VAR}$$

$$\mathbf{S}_2 = 1.2 + \mathrm{j}0 \; \mathrm{kVA}$$

$$P_3 = (10)(120) = 1.2 \text{ kW}$$
,  $Q_3 = 0 \text{ VAR}$ 

$$\mathbf{S}_3 = 1.2 + \mathrm{j}0 \; \mathrm{kVA}$$

$$Q_4 = 1.6 \text{ kVAR}$$
,  $\cos \theta_4 = 0.6 \longrightarrow \sin \theta_4 = 0.8$ 

$$S_4 = \frac{Q_4}{\sin \theta_4} = 2 \text{ kVA}$$

$$P_4 = S_4 \cos \theta_4 = (2)(0.6) = 1.2 \text{ kW}$$
  
 $S_4 = 1.2 - \text{j}1.6 \text{ kVA}$ 

$$S = S_1 + S_2 + S_3 + S_4$$
  
 $S = 7.3285 + j1.196 \text{ kVA}$ 

Total real power = 7.3285 kWTotal reactive power = 1.196 kVAR

(b) 
$$\theta = \tan^{-1} \left( \frac{1.196}{7.3285} \right) = 9.27^{\circ}$$

$$pf = \cos \theta = \underline{\mathbf{0.987}}$$

## Chapter 11, Solution 94


$$\begin{aligned} \cos\theta_1 &= 0.7 & \longrightarrow & \theta_1 &= 45.57^\circ \\ S_1 &= 1 \text{ MVA} = 1000 \text{ kVA} \\ P_1 &= S_1 \cos\theta_1 = 700 \text{ kW} \\ Q_1 &= S_1 \sin\theta_1 = 714.14 \text{ kVAR} \end{aligned}$$

For improved pf,

$$\cos \theta_2 = 0.95 \longrightarrow \theta_2 = 18.19^{\circ}$$
  
 $P_2 = P_1 = 700 \text{ kW}$ 

$$S_2 = \frac{P_2}{\cos \theta_2} = \frac{700}{0.95} = 736.84 \text{ kVA}$$
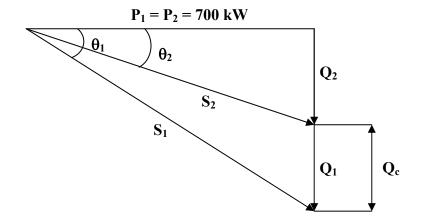
$$Q_2 = S_2 \sin \theta_2 = 230.08 \text{ kVAR}$$



(a) Reactive power across the capacitor  $Q_c = Q_1 - Q_2 = 714.14 - 230.08 = 484.06 \text{ kVAR}$ 

Cost of installing capacitors =  $$30 \times 484.06 = $14,521.80$ 

(b) Substation capacity released = 
$$S_1 - S_2$$
  
=  $1000 - 736.84 = 263.16 \text{ kVA}$ 

Saving in cost of substation and distribution facilities  $= $120 \times 263.16 = $31,579.20$ 

(c) <u>Yes</u>, because (a) is greater than (b). Additional system capacity obtained by using capacitors costs only 46% as much as new substation and distribution facilities.

# Chapter 11, Solution 95

(a) Source impedance 
$$\mathbf{Z}_s = \mathbf{R}_s - j\mathbf{X}_c$$
  
Load impedance  $\mathbf{Z}_L = \mathbf{R}_L + j\mathbf{X}_2$ 

For maximum load transfer

$$\mathbf{Z}_{L} = \mathbf{Z}_{s}^{*} \longrightarrow \mathbf{R}_{s} = \mathbf{R}_{L}, \quad \mathbf{X}_{c} = \mathbf{X}_{L}$$


$$\mathbf{X}_{c} = \mathbf{X}_{L} \longrightarrow \frac{1}{\omega \mathbf{C}} = \omega \mathbf{L}$$

or 
$$\omega = \frac{1}{\sqrt{LC}} = 2\pi f$$

$$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(80\times10^{-3})(40\times10^{-9})}} = \frac{2.814 \text{ kHz}}{2\pi\sqrt{(80\times10^{-3})(40\times10^{-9})}}$$

(b) 
$$P = \frac{V_s^2}{4R_A} = \frac{(4.6)^2}{(4)(10)} = \underline{529 \text{ mW}}$$
 (since  $V_s$  is in rms)

## Chapter 11, Solution 96

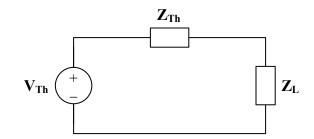

(a) 
$$\begin{aligned} V_{\text{Th}} &= 146 \text{ V}, \quad 300 \text{ Hz} \\ Z_{\text{Th}} &= 40 + j8 \, \Omega \end{aligned}$$

$$Z_{\rm L} = Z_{\rm Th}^* = \underline{\mathbf{40 - j8\,\Omega}}$$

(b) 
$$P = \frac{|V_{Th}|^2}{8R_{Th}} = \frac{(146)^2}{(8)(40)} = \underline{\mathbf{66.61 W}}$$

## Chapter 11, Solution 97

$$Z_T = (2)(0.1 + j) + (100 + j20) = 100.2 + j22 \Omega$$

$$I = \frac{V_s}{Z_T} = \frac{240}{100.2 + i22}$$

$$P = |I|^2 R_L = 100 |I|^2 = \frac{(100)(240)^2}{(100.2)^2 + (22)^2} = \underline{547.3 \text{ W}}$$